

### HW 3

Posted Monday 2/13/2012

Due **Wednesday** 2/22/2012


EE40

Maharbiz

Spring 2012


If you're taking EE105 next semester, you'll thank me for problems 1 and 2. ☺

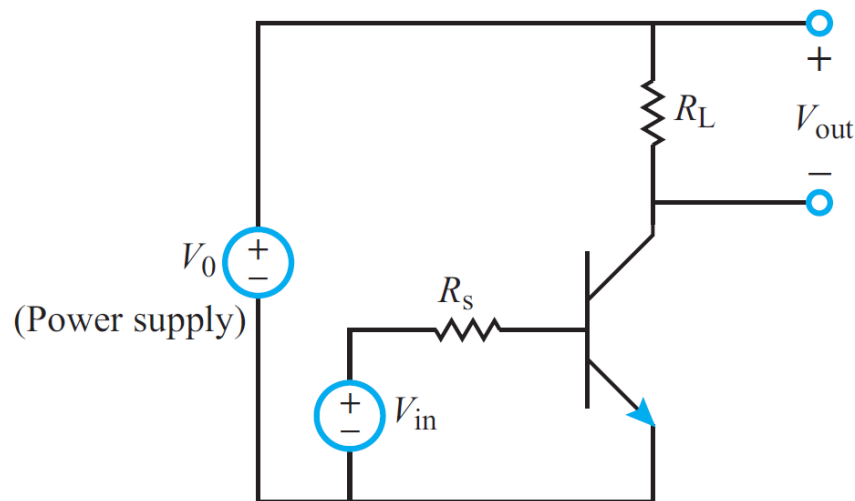1. The circuit below is a BJT *common emitter amplifier*. Find  $V_{out}$  as a function of  $V_{in}$ . This may seem hard to parse at first, but it is actually pretty straightforward. Carefully replace the BJT symbol with the model for a BJT we used in class, making sure the base (B), emitter (E), and collector (C) terminals are connected properly, then use any method you want to solve for  $V_{out}$ !



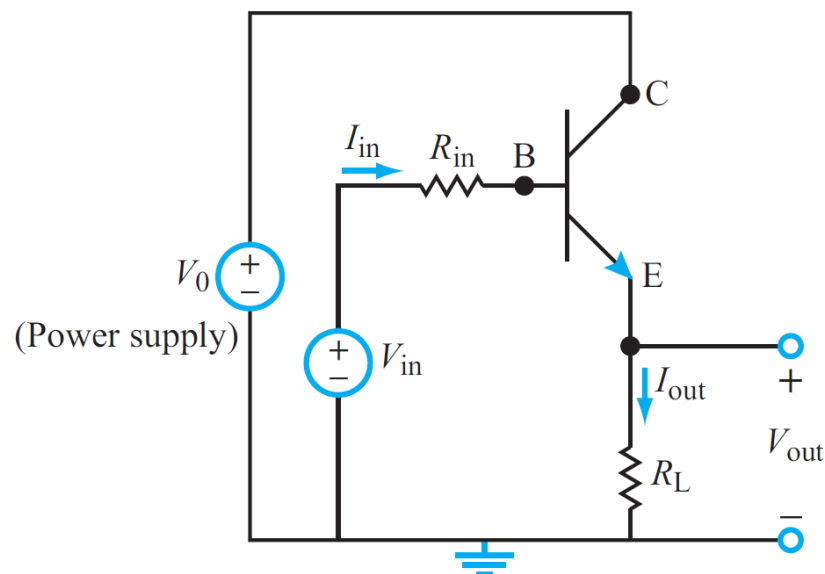
2. The circuit below is a BJT *common collector amplifier*. Find both the voltage gain ( $A_V = V_{out} / V_{in}$ ) and the current gain ( $A_I = I_{out} / I_{in}$ ). As with Problem 1, this may seem hard to parse at first, but it is actually pretty straightforward. Carefully replace the BJT symbol with the model for a BJT we used in class, making sure the base (B), emitter (E), and collector (C) terminals are connected properly, then use any method you want to solve for  $V_{out}$ !

For this problem, you can assume  $V_{in} \gg V_{BE}$ .




3. In the circuit shown below, a potentiometer is connected across the load resistor  $R_L$ . The total resistance of the potentiometer is  $R = R_1 + R_2 = 5 \text{ k}\Omega$ .

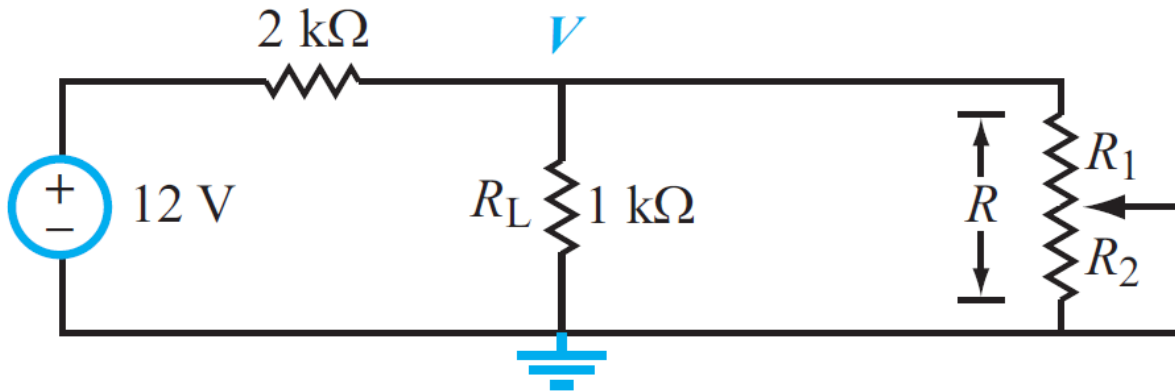- (a) Obtain an expression for the power  $P_L$  dissipated in  $R_L$  for any value of  $R_1$ .  
 (b) Plot  $P_L$  versus  $R_1$  over the full range made possible by the potentiometer's wiper.




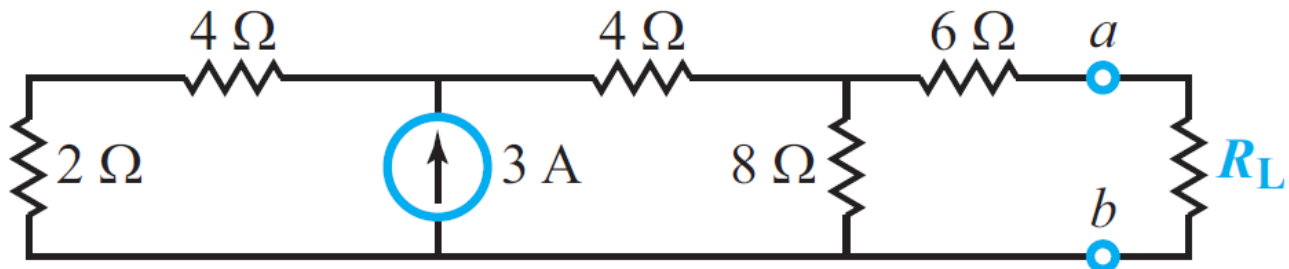4. a) What value of the load resistor  $R_L$  will extract the maximum amount of power from the circuit below?  
 b) How much power will that be?

**Hint:** you need to use both the concepts of Thevenin equivalent circuits and maximum power transfer.



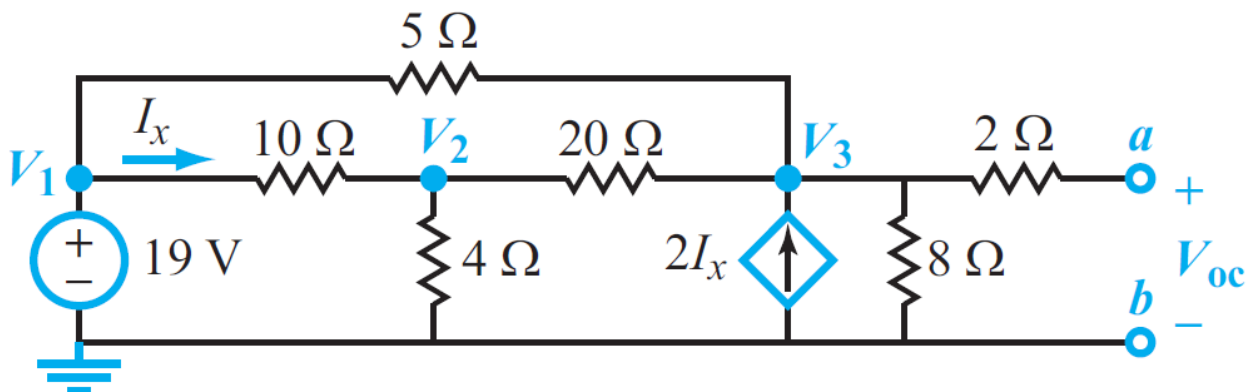5. Find the Thevenin equivalent circuit at terminals (a,b) of the circuit below:



6. Find the Norton equivalent circuit of the circuit.

