

YOUR NAME:

YOUR SID:

YOUR PARTNER'S NAME:

YOUR PARTNER'S SID:

Pre-Lab: __/10

Lab: __/90

Total: __/100

Filters

LAB 6: Filters

ELECTRICAL ENGINEERING 40

INTRODUCTION TO MICROELECTRONIC CIRCUITS

University Of California, Berkeley

Department of Electrical Engineering and Computer Sciences

Professor Michel Maharbiz, Professor Vivek Subramanian, Vincent Lee, Linda Dai

Lab Contents:

- I. Lab Objectives
- II. Pre-Lab Component
 - a. Background and Theory
 - b. Voltage Dividers and Filters
- III. Lab Component
 - a. Passive Low Pass Filters
 - b. Passive High Pass Filters
 - c. Active Filters
- IV. Lab Submissions
 - a. Image Citations

Lab Objectives


Filters have a wide range of applications and can be found in many electronic devices. Such applications include a low pass filter in your telephone land line and a high pass filter for your high bandwidth DSL modem, a band pass filter in your cell phone so that you only hear the person on the other line and not everyone else around you using their cell phones, a band reject filters to reject the 50 Hz or 60 Hz AC power signal when using very sensitive components, and many other applications in audio processing, communications, sensors, etc. For our EEG final project, we will be using filters to eliminate noise while passing the low frequency brain wave signal we want to capture.

In this lab we will be designing several different types of filters using passive components such as resistors, capacitors, and inductors. Specifically we will be implementing passive and active filters which each have their advantages and disadvantages.

Pre-Lab Component

Background and Theory

As you may recall, each passive circuit component (resistor, inductor, and capacitor) can be abstracted in terms of complex resistances. So far you have been working with DC current where the supply voltages are constant. When the supply voltages to the circuit are constant and the circuit has reached equilibrium, we know that resistors simply act as attenuators, capacitors act as open circuits, and inductors act as short circuits.

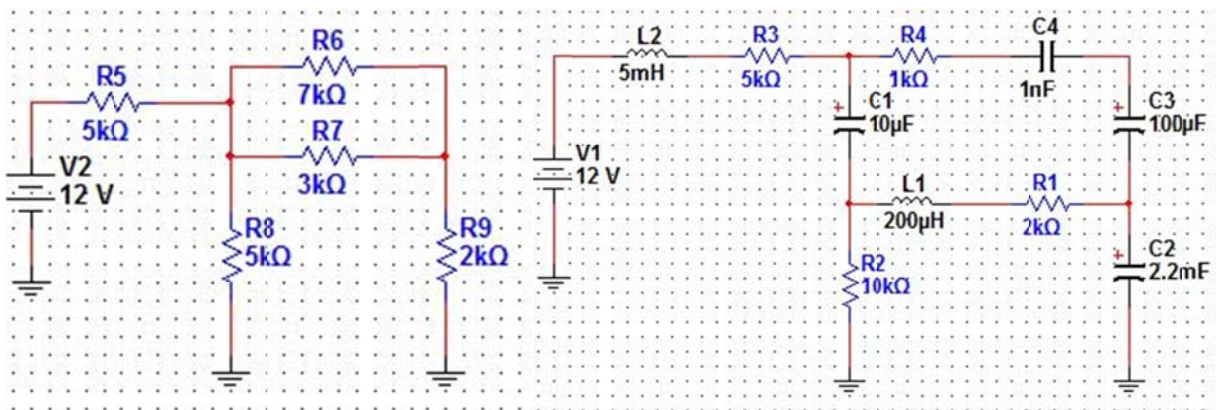

Purely Resistive Network on Left, RLC Network on Right

In addition, we can use simple voltage division to find the value of the voltage at each node.

The behavior of such passive circuit networks changes when a variable voltage supply is put into the system. For example, if we applied a sinusoidal input to a circuit network, we would observe different circuit behavior because of the equations that govern capacitors and inductors. Recall that the equations that relate voltage and current for each passive component are given as follows:

Resistor $V = IR$	Capacitor $I = C \left(\frac{dV}{dt} \right)$	Inductor $V = L \left(\frac{dI}{dt} \right)$
----------------------	---	--

So for constant voltages such that $V = V_0$, we obtain:

Resistor $I = \frac{V_0}{R}$	Capacitor $I = C \left(\frac{d}{dt} V_0 \right) = 0$	Inductor $I = \int \frac{V_0}{L} dt + I_{init}$
---------------------------------	--	--


And for constant current such that $I = I_0$ we obtain:

Resistor $V = I_0 R$	Capacitor $V = \int \frac{I_0}{C} dt + V_{init}$	Inductor $V = L \left(\frac{d}{dt} I_0 \right) = 0$
-------------------------	---	---


Now let's consider what happens when we apply a sinusoidal input, supposed the input signal is given by $V(t) = V_0 \sin(\omega t)$:

Resistor $I(t) = \frac{V_0 \sin(\omega t)}{R}$	Capacitor $I(t) = C \left(\frac{d}{dt} V_0 \sin(\omega t) \right) = \omega C V_0 \cos(\omega t)$	Inductor $I(t) = \int \frac{V_0 \sin(\omega t)}{L} dt = -\frac{V_0 \cos(\omega t)}{\omega L}$
---	--	--

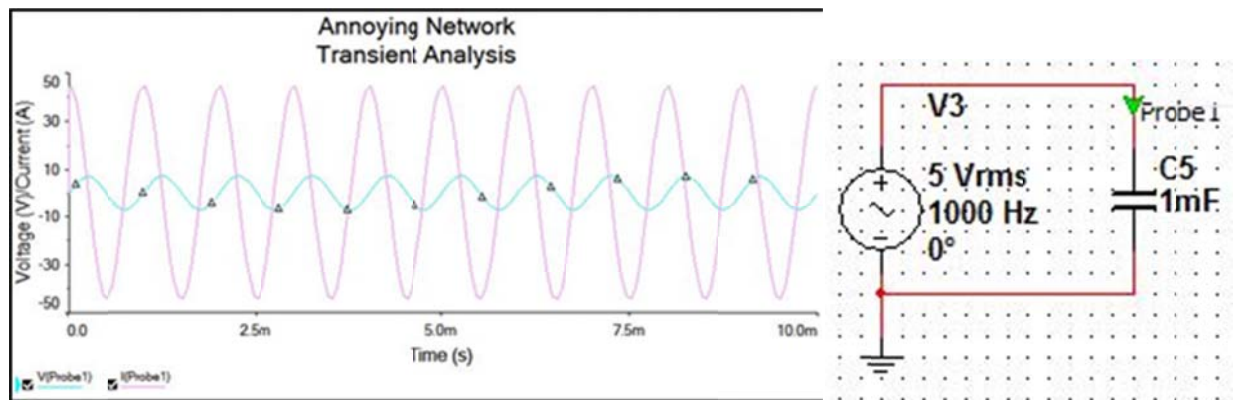From here it's easy to see that the current for the capacitor and inductors are not in phase with the voltage signal. For the resistor we see that the current is just attenuated by a factor of the resistance so we simply get Ohm's Law.



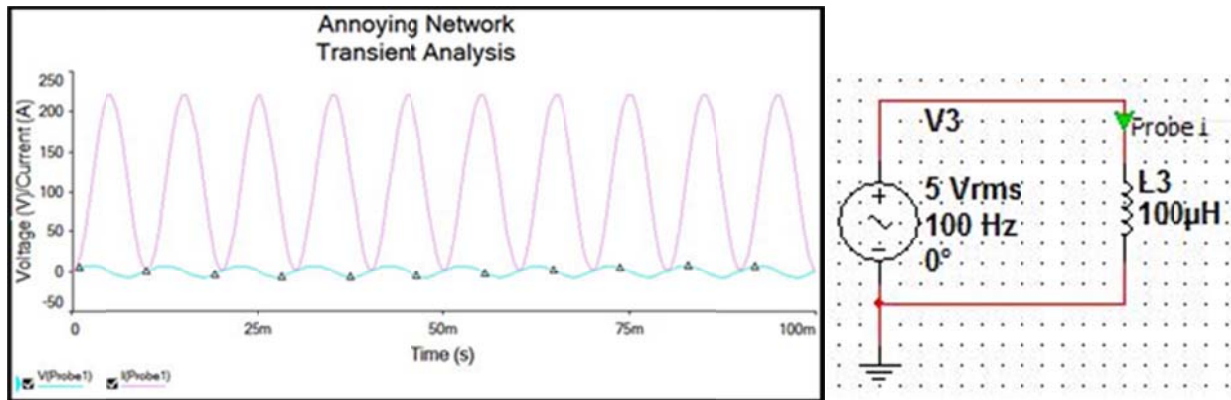The figure above shows a transient analysis of the capacitor circuit at Probe 1. The blue line indicates the voltage signal and the pink line indicates the current. For the capacitor we see that the voltage is 90 degrees out of phase with the current and the voltage lags behind the current. In this case, we say that the voltage **lags** the current or the current **leads** the voltage.



The figure above shows the transient analysis of an inductor network. Again, the blue line indicates voltage and the pink line indicates current. For the inductor we see that the voltage and current are once again 90 degrees out of phase, but the voltage **leads** the current or the current **lags** behind the voltage.

Now that we've established the relationship between the voltage and current for various circuit components, we have a clearer intuition from where the complex phasor representation comes from. From your reading, you should have already seen that each passive component can be modeled as a complex resistor.

Recall that in phasor analysis, multiplication by the imaginary number j represents a 90 degree rotation with no change in magnitude and dividing by j gives a -90 degree rotation.¹ From what we have seen above, we can see that using j we can represent the relationships between voltage and current for capacitors and inductors.

These complex resistances are referred to as **impedance** often denoted by the letter Z . The impedance of the passive circuit components that you are familiar with are given below. Notice that the impedance for the capacitor and inductor are dependent on the angular frequency ω of the waveform.

Impedance of Resistor	Impedance of Capacitor	Impedance of Inductor
$Z_R = R$	$Z_C = \frac{1}{j\omega C}$	$Z_L = j\omega L$

Also notice that for $\omega = 0$ which corresponds to a DC constant, these impedances converge to what you would expect. The impedance of the capacitor goes to ∞ , which corresponds to an open circuit, and the impedance of the inductor goes to 0, which denotes a short circuit.

Now that we have a complex representation for each component, we can treat capacitors and inductors as resistors and apply the same principles as before such as voltage division and nodal analysis.


In the next section, we will explore how to apply these analysis techniques to filters.

¹ We use j as the complex units since i is already taken for current

Voltage Dividers and Filters

Now that we've established how to break down complicated passive circuit networks into a network of complex resistors, we can simply apply the basic principles pertaining to resistive networks as we did in lab 2. Techniques such as voltage divider and node voltage analysis still apply to resistive networks with complex resistors or impedances.

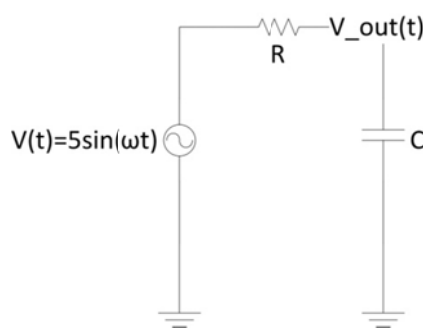For instance, consider the network below. The circuit network below is an RC circuit. When we apply a DC current to this network, we see that the capacitor simply acts as an open circuit and the voltage between the resistor and capacitor with an applied voltage V across the network is simply V after a very long time.



But what if we wanted to apply a sinusoidal voltage signal such as $V(t) = 5\sin(\omega t)$ across the network? We find that we can use the voltage division law using the impedances of each component to find the voltage signal at the intermediate node. Furthermore, after some calculations, we find that the resulting signal is frequency dependent since the impedance of the capacitor is frequency dependent.


In the space below, show that the voltage signal $V_{out}(t)$ at the node between the resistor and capacitor is:

$$V_{out}(t) = \frac{5\sin(\omega t)}{j\omega RC + 1}$$

Notice that in this expression that the signal at the intermediate node $V_{out}(t)$ is a factor of $\frac{1}{j\omega RC + 1}$ times the input voltage signal $V(t)$. We call such systems that produce a scaled input as its output a **linear system**. If we further manipulate the expression to eliminate the time dependence, we can solve for an expression in terms of the just the frequency ω given by $\frac{V_{out}}{V}(\omega)$.

$$V_{out}(t) = \frac{5 \sin(\omega t)}{j\omega RC + 1} \rightarrow \frac{V_{out}(t)}{5 \sin(\omega t)} = \frac{1}{j\omega RC + 1} \rightarrow \frac{V_{out}}{V}(\omega) = \frac{1}{j\omega RC + 1}$$

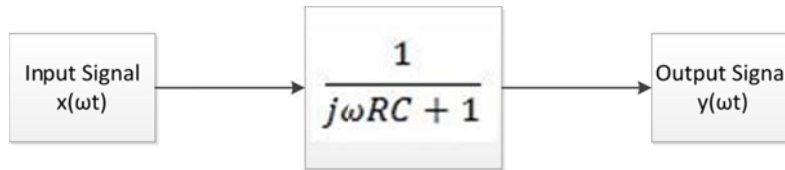We call this expression the **frequency response** of the circuit which we can use to determine the scaling of the input signal for a given frequency. In EECS 20N, you may have seen something like this:



Now let's consider the frequency response expression that we derived for this network. Since the expression is frequency dependent, we can postulate that the circuit is some sort of filter. Quite often we are interested in how this circuit network passes or attenuates different frequencies so we plot the frequency against the magnitude and the frequency against the phase. From your algebra and pre-calculus class, you know that the expression we derived for this filter network resembles the function $\frac{1}{x}$. However, this expression is difficult to plot and read because of its exponential nature.

To cure this eyesore and cleanly exhibit the properties of filter networks we use a Bode plot. The Bode plot generally uses ω on the x-axis, which is plotted on the log scale, and another value for the y-axis, usually the magnitude or the phase. For those of you who have taken EECS 20N, the Bode plot is simply the circuit guru version of the **magnitude response plot** and the **phase response plot**. The only differences are that the Bode plot uses a logarithmic scaling factor using decibels (dB) as units for magnitude. Phase is generally plotted in degrees. A few example Bode plots are here: http://en.wikipedia.org/wiki/Bode_plot

Given a frequency response function $H(\omega)$, the magnitude response is given by $|H(\omega)|$ and the phase response is given by $\arg(H(\omega))$. You can brush up on your complex numbers here: http://en.wikipedia.org/wiki/Complex_number#Absolute_value_and_argument


The decibel conversion is given by:

$$\text{Magnitude response in decibels} = 20 \cdot \log(\text{Magnitude response})$$

Note that the decibel and magnitude response are both unitless. Also notice that we use a factor of 20 instead of a factor of 10 as you might have seen in the measurement of sound wave amplitude. This extra factor of 2 is because the equation for power in circuits is given by:


$$P = IV \rightarrow I = \frac{V}{R} \rightarrow P = \frac{V^2}{R} \rightarrow P \propto V^2 \rightarrow 10 \log\left(\frac{P}{P_{ref}}\right) = 10 \log\left(\frac{V^2}{V_{ref}^2}\right) = 20 \log\left(\frac{V}{V_{ref}}\right)$$

 Using the decibel conversion given above, and the expression we derived for $\frac{V_{out}}{V}(\omega)$, draw the Bode plot (**both magnitude and phase**) in the space provide below. Clearly label your axes and increments and indicate any relevant points on the graph in terms of the variables V_{out} , V , ω , R , and C .




For your Bode plot, you should have found that the circuit network attenuates higher frequencies at a rate of 20 dB per decade. Such circuit systems that pass lower frequencies are said to pass lower frequencies and are known as **low pass filters (LPF)**.

You will notice on the Bode plot, that there is an initial plateau before the frequency $\omega = \frac{1}{RC}$ following by a -20dB per decade decrease. The filter therefore still passes some of the higher frequency parts of the spectrum which may sometimes be undesirable. To minimize the amount of higher frequency signals passed by the filter, we cascade two or more of the same filter shown below.

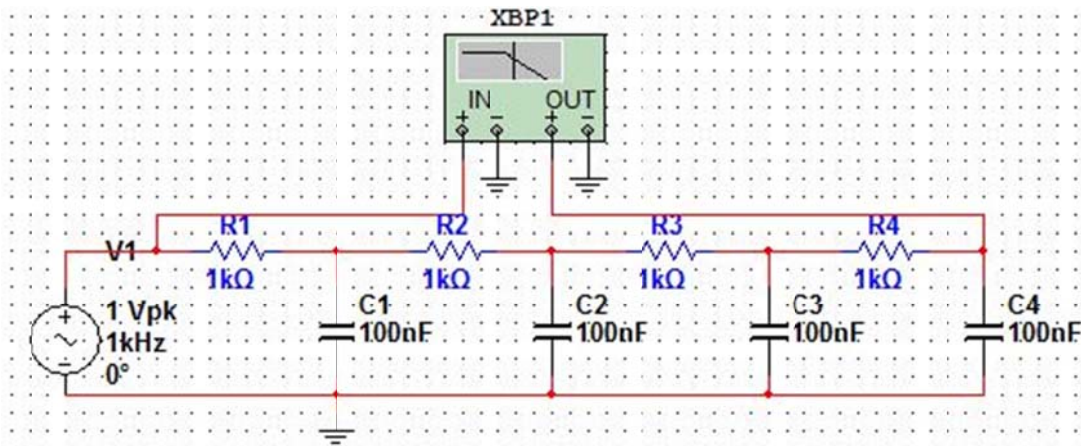

A Fourth Order Passive Low Pass Filter – The Virtual Instrument XBP1 is a Bode Plotter.


The Bode plot is shown below.

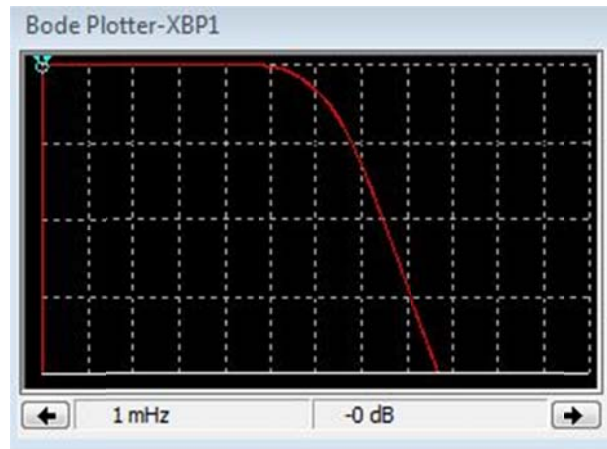

Magnitude Response Plot of Fourth Order LPF

For those of you who are familiar with signals and systems, the fourth order LPF looks like two systems cascaded in series of which the frequency response is given by the multiplication of the two individual frequency responses of each LPF.

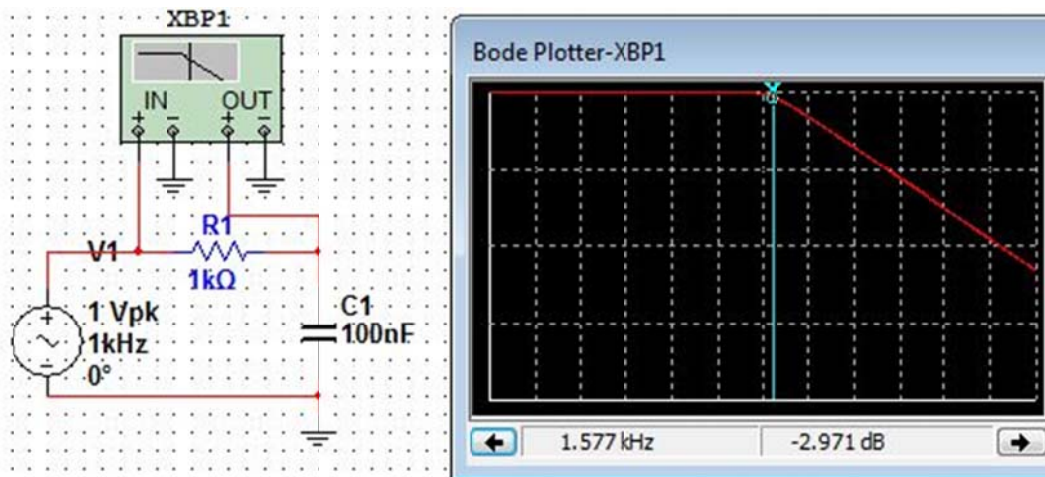If we compare this to the first order LPF shown below, we see the slope drops off much faster in the fourth order LPF.



First Order Passive LPF Circuit and Associated Magnitude Response Plot

Lab Component

A common application of filters is to eliminate undesired frequencies such as high frequency noise or low frequency DC components. In music applications, we may want to extract certain frequency bands, boost bass, or keep only high frequencies for various different types of audio processing techniques.

The most common filters that you will encounter are the low pass, high pass, band pass, and band reject filters. Many other filters also exist, however, the mathematical analysis required to design those filters is out of the scope of this course (see EE120). As was discussed earlier, these filters can also be active or passive.

In the first part of the lab, we will start with the passive filters and move onto active filters. In particular, we want to pay attention to the low pass filters since those will be what we will be implementing on our EEG.

Passive Low Pass Filters

In audio applications, it is important to eliminate any stray high frequency content which can potentially damage your hearing. Thus, it is common practice to liberally apply low pass filters to kill these undesired frequencies. So how do we do that?

We know that the audible hearing range spans from about 20 Hz to 20000 Hz so we'll start with that. In the space provided below or a separate sheet of paper, design a passive low pass filter such that the cutoff frequency will adequately attenuate the high frequencies and pass the low frequencies. Explain all calculations and draw the Bode plot (both magnitude and phase) for your filter. Hint: Remember ω has units of rad/s, f has units of Hz, and $\omega = 2\pi f$.

Score __/15

More workspace...

Now that we have our low pass filter, we will now see if it works. Before we apply the corrupted signal, we will test our filter using the function generator.

For starters, first build your circuit and make sure to note where the input voltage signal and the output voltage signal should be.

Turn on your function generator and make sure that it is a sinusoidal waveform. You may also want to set the peak-to-peak voltage to something like 5V.

Connect the function generator to the input of the filter and ground.

Now turn on your oscilloscope. We will be using this to observe the attenuation of the input waveform by comparing it to the output waveform.

Connect one scope to the input of the filter and measure the peak-to-peak value of the input waveform.

Connect the other scope to the output of the filter and measure the peak-to-peak value of the output waveform.

At this point, your set up should show two waveforms on the oscilloscope of the same frequency (try auto-scaling if you don't). You should also have two peak-to-peak measurements active on your oscilloscope. If you don't make sure to hit Voltage and V-pp to get the peak-to-peak measurements.

We can now verify if our filter is working properly. To do this, let's change the frequency of the input waveform by adjusting the function generator. By doing this, we can sweep a range of frequencies, check the attenuation, and verify if it matches our Bode plot.

Take your function generator and set the frequency to 1 Hz. (This is essentially a constant signal).

Check the peak-to-peak value of the input and the peak-to-peak value of the output.

Calculate the attenuation (or amplification) and verify that it matches your predict value on your Bode plot.

Repeat this at 10 x increments (i.e., increase the frequency ten times for each measurement). **Record your measurements** in the table provided below. If your values tend to deviate too far from predicted values, you may want to verify your calculations. **(5 pts)**

Frequency	Peak-to-peak value of input	Peak-to-peak value of output	Gain/Attenuation Factor	Gain/Attenuation in dB
1 Hz				
10 Hz				
100 Hz				
1 kHz				
10 kHz				
100 kHz				
1 MHz				
10 MHz				

Passive High Pass Filters

Now suppose we wanted a passive high pass filter that rejected frequencies below 1000Hz. In the space provided below, design a passive high pass filter and prove that adequately rejects frequencies below the appropriate cutoff frequency. Also explain all calculations and provide a Bode plot (both magnitude and phase).

Score: __/10

More workspace...

Now suppose you put your low pass filter with the high pass filter together (i.e., the output of the low pass filter is the input to the high pass filter) (You don't have to actually do this). Neglecting any interaction between the filters, what type of filter do you get? If we hacked a microphone with this filter, do you think a man or a woman would be more understandable when speaking through the mike?

Score: __/5

Active Filters


In the previous parts, we have been using what we call passive components (resistors, capacitors, and inductors) to implement our filters. We call these filters passive because they do not require a power source to operate. Consequently, these filters can only pass or attenuate the input signals, and may require a separate amplification stage.

An alternative to passive filters are active filters. Typically, an active filter will use one or more operational amplifiers to amplify the signal and filter it at the same time. For our EEG project, we will be designing a filter that will adequately attenuate high frequencies but amplify and pass low frequencies below a certain threshold.

There are many different way to implement an active low pass filter but all active filters, as the name implies, use an active circuit element such as an operation amplifier. For this portion of the lab we will supply you with the necessary circuit. It will be your job to figure out how it works.

Note that the maximum gain of this circuit is not limited to 1 unlike passive filters.

Below is the circuit schematic for an active low pass filter:

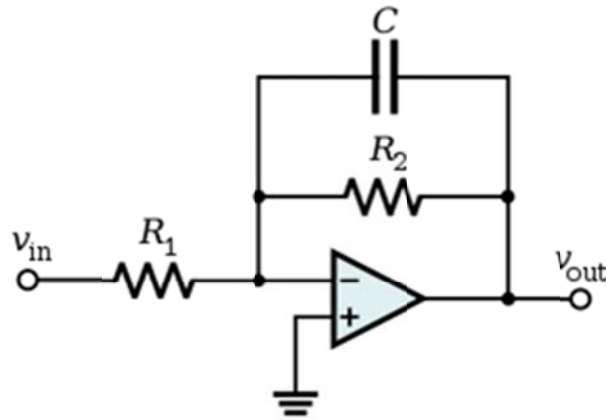First Order Active Low Pass Filterⁱ

In the space provided below, find an expression for the frequency response of this system, and prove that the maximum gain of the active low pass filter G_{low} and the cutoff frequency ω_c are given by the following:

$$G_{low} = -\frac{R_2}{R_1} \text{ and } \omega_c = \frac{1}{R_2 C}$$

In addition, draw the Bode plots of the magnitude and phase responses of the active low pass filter circuit, and clearly label important point on your plots in terms of the given variables and appropriate constants.

More workspace...

Now that you have a better idea of what's going on, choose components values such that the cutoff frequency for your active low pass filter is 100Hz and the maximum gain is approximately 10. Then implement your active low pass filter and fill out the following measurements as you did with the passive filters in the previous parts. **(5 pts)**

Frequency	Peak-to-peak value of input	Peak-to-peak value of output	Gain/Attenuation Factor	Gain/Attenuation in dB
1 Hz				
10 Hz				
100 Hz				
1 kHz				
10 kHz				
100 kHz				
1 MHz				
10 MHz				

Show your active filter set up to your GSI for check off. Make sure you are able to demonstrate and explain why your filter works using your scope.

Your GSI Signs Here **(35 pts)**

Lab Report Submissions

This lab is **due at the beginning** of the next lab section. Make sure you have **completed all questions** and **drawn all the diagrams** for this lab. In addition, attach any loose papers specified by the lab and submit them with this document.

These labs are designed to be completed in **groups of two**. Only one person in your team is required to submit the lab report. Make sure the names and student IDs of **BOTH** team members are on this document (preferably on the front).

Image Citations

ⁱ http://upload.wikimedia.org/wikipedia/commons/5/59/Active_Lowpass_Filter_RC.svg