

**Problem 5.7** After opening a certain switch at  $t = 0$  in a circuit containing a capacitor, the voltage across the capacitor started decaying exponentially with time. Measurements indicate that the voltage was 7.28 V at  $t = 1$  s and 0.6 V at  $t = 6$  s. Determine the initial voltage at  $t = 0$  and the time constant of the voltage waveform.

**Solution:**

$$v(t) = v_0 e^{-t/\tau} \quad (\text{V}).$$

$$7.28 = v_0 e^{-1/\tau}$$

$$0.6 = v_0 e^{-6/\tau}$$

$$\frac{7.28}{0.6} = \frac{e^{-1/\tau}}{e^{-6/\tau}} = e^{5/\tau}$$

$$\ln\left(\frac{7.28}{0.6}\right) = \frac{5}{\tau}$$

$$\tau = \frac{5}{2.5} = 2.$$

$$7.28 = v_0 e^{-1/2} = 0.61 v_0$$

$$v_0 = \frac{7.28}{0.61} = 12 \text{ V}.$$

$$v(t) = 12e^{-0.5t} \quad (\text{V}).$$

**Problem 5.12** The current through a  $40\text{-}\mu\text{F}$  capacitor is given by a rectangular pulse as

$$i(t) = 40\text{rect}\left(\frac{t-1}{2}\right) \text{ mA}.$$

If the capacitor was initially uncharged, determine  $v(t)$ ,  $p(t)$ , and  $w(t)$ .


**Solution:** For  $0 \leq t \leq 2$ ,

$$\begin{aligned} v(t) &= v(0) + \frac{1}{C} \int_0^t i \, dt \\ &= 0 + \frac{1}{40 \times 10^{-6}} \int_0^t 40 \times 10^{-3} \, dt \\ &= 1000t \quad (\text{V}). \end{aligned}$$

Hence,

$$\begin{aligned} v(t) &= \begin{cases} 0 & \text{for } t < 0 \\ 1000t \text{ (V)} & \text{for } 0 \leq t \leq 2 \text{ s} \\ 2000 \text{ (V)} & \text{for } t \geq 2 \text{ s} \end{cases} \\ p(t) &= i(t) v(t) \\ &= \begin{cases} 0 & \text{for } t < 0 \\ 40t \text{ (A)} & \text{for } 0 \leq t \leq 2 \text{ s} \\ 0 & \text{for } t > 2 \text{ s} \end{cases} \\ w(t) &= \frac{1}{2} C v^2 = \begin{cases} 0 & \text{for } t < 0 \\ 20t^2 \text{ (mJ)} & \text{for } 0 \leq t \leq 2 \text{ s} \\ 80 \text{ (mJ)} & \text{for } t \geq 2 \text{ s} \end{cases} \end{aligned}$$

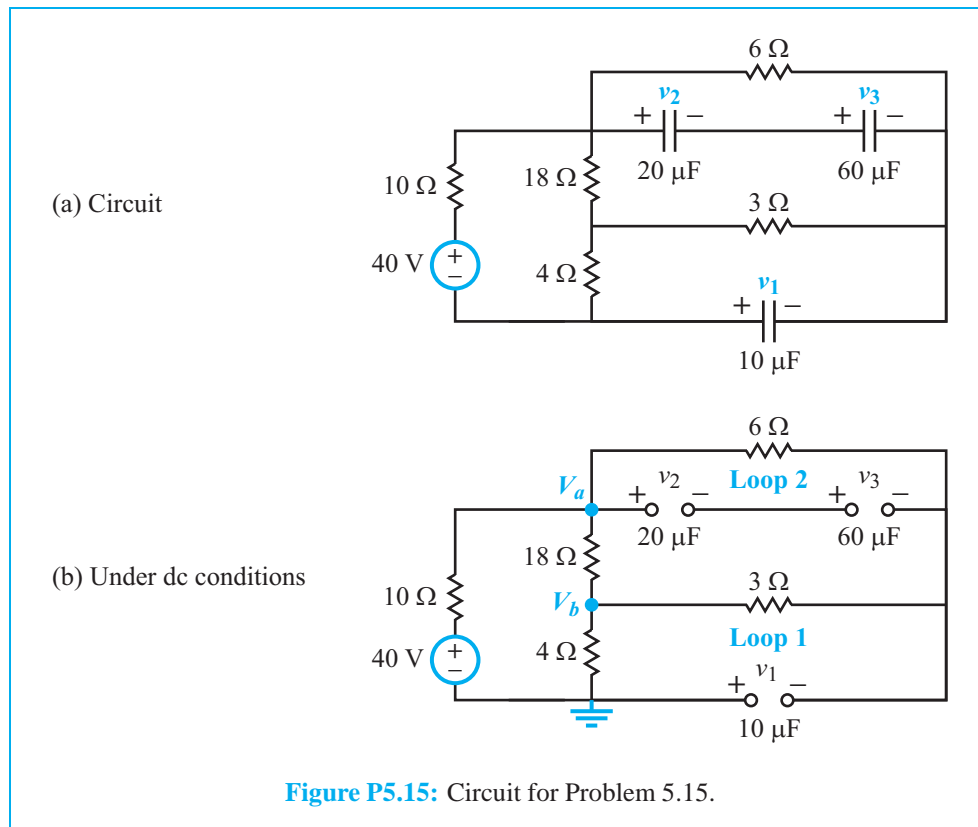**Problem 5.15** Determine voltages  $v_1$  to  $v_3$  in the circuit of Fig. P5.15 under dc conditions.



**Solution:** KCL at nodes  $V_a$  and  $V_b$ :

$$\frac{V_a - 40}{10} + \frac{V_a - V_b}{18} + \frac{V_a - V_b}{6 + 3} = 0$$

$$\frac{V_b}{4} + \frac{V_b - V_a}{18} + \frac{V_b - V_a}{6 + 3} = 0$$

Solution gives

$$V_a = 20 \text{ V}, \quad V_b = 8 \text{ V}.$$

For Loop 1,

$$-v_1 - V_b + (V_b - V_a) \frac{3}{9} = 0,$$

which gives

$$v_1 = -12 \text{ V}.$$

For Loop 2,

$$-v_3 - v_2 + (V_a - V_b) \frac{6}{9} = 0$$

which gives

$$v_3 + v_2 = (20 - 8) \frac{6}{9} = 8 \text{ V}. \quad (1)$$

For two capacitors in series, Eq. (5.47) gives

$$v_2 C_2 = v_3 C_3$$

or

$$20v_2 = 60v_3 \quad (2)$$


Simultaneous solution of Eqs. (1) and (2) leads to

$$v_2 = 6 \text{ V}, \quad v_3 = 2 \text{ V}.$$

**Problem 5.21** Assume that a 120-V dc source is connected at terminals  $(a,b)$  to the circuit in Fig. P5.17. Determine the voltages across all capacitors.


**Solution:** We first simplify the circuit to find  $C_{eq}$  at terminals  $(a,b)$ , and then we work backwards to determine the voltages across the capacitors.

**Step 1:** Find  $C_{eq}$ .

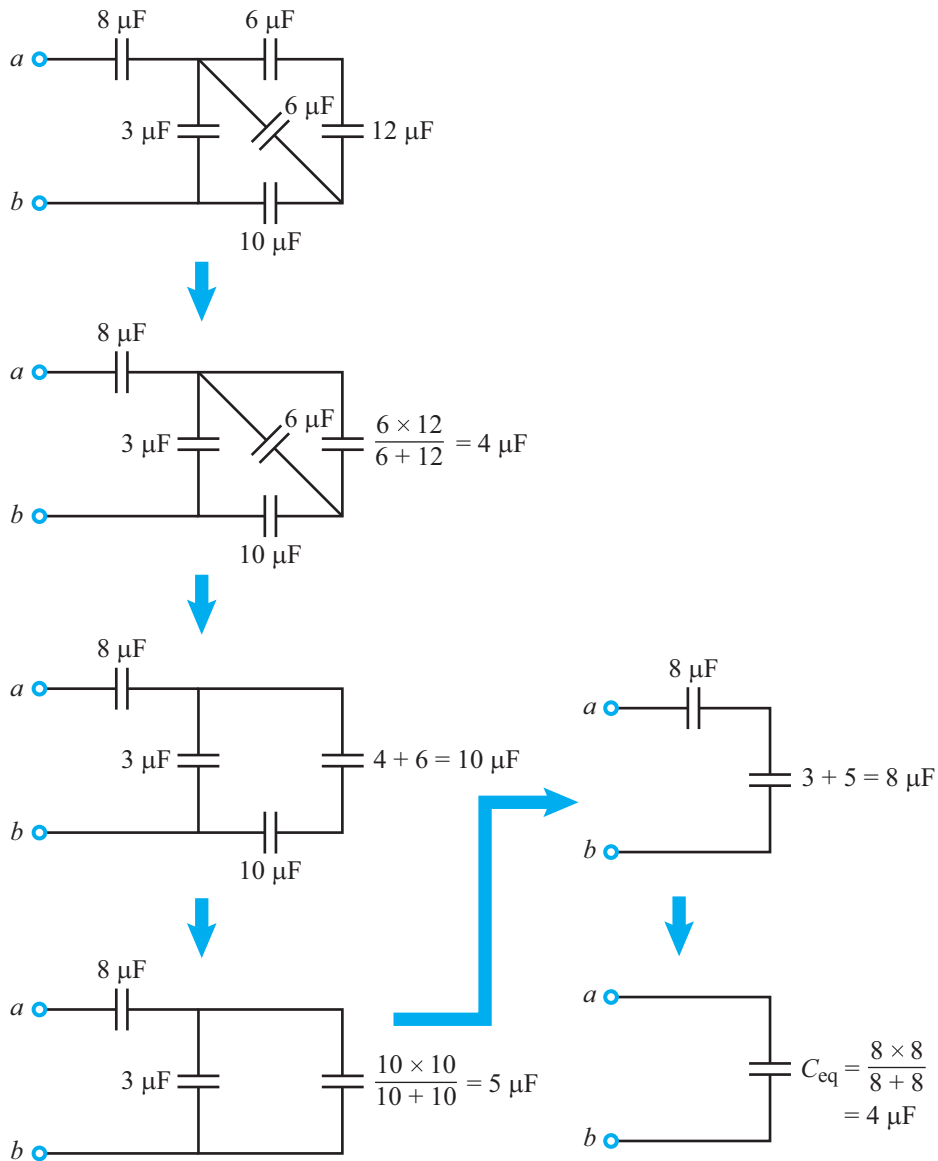

**Step 2:** Find voltages.

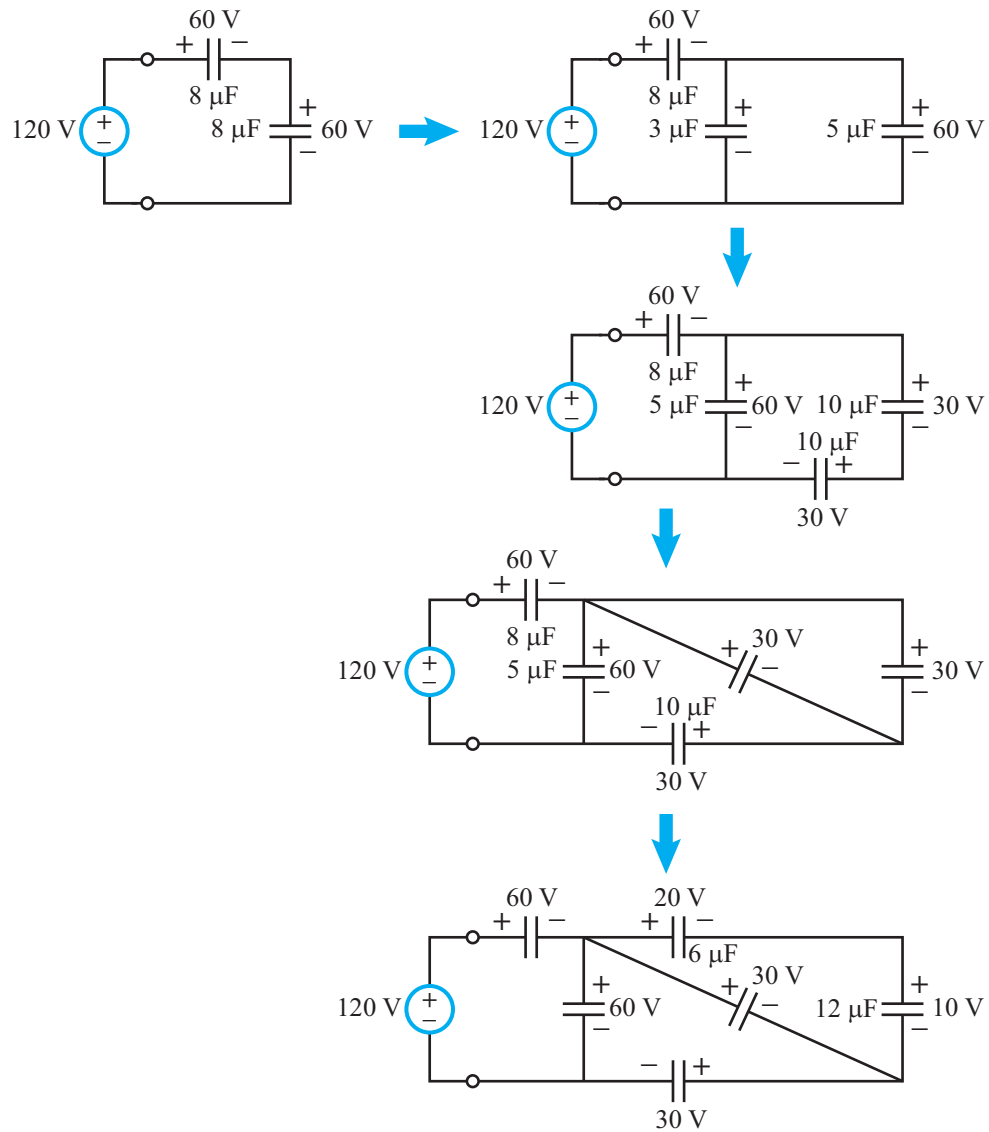- Two capacitors in parallel share the same voltage.
- For two capacitors in series:  $C_1 v_1 = C_2 v_2$ .



**Problem 5.35** The circuit in Fig. P5.35 contains two switches, both of which had been open for a long time before  $t = 0$ . Switch 1 closes at  $t = 0$ , and switch 2 follows suit at  $t = 5$  s. Determine and plot  $v_C(t)$  for  $t \geq 0$  given that  $V_0 = 24$  V,  $R_1 = R_2 = 16$  k $\Omega$ , and  $C = 250$   $\mu$ F. Assume  $v_C(0) = 0$ .

**Solution:**

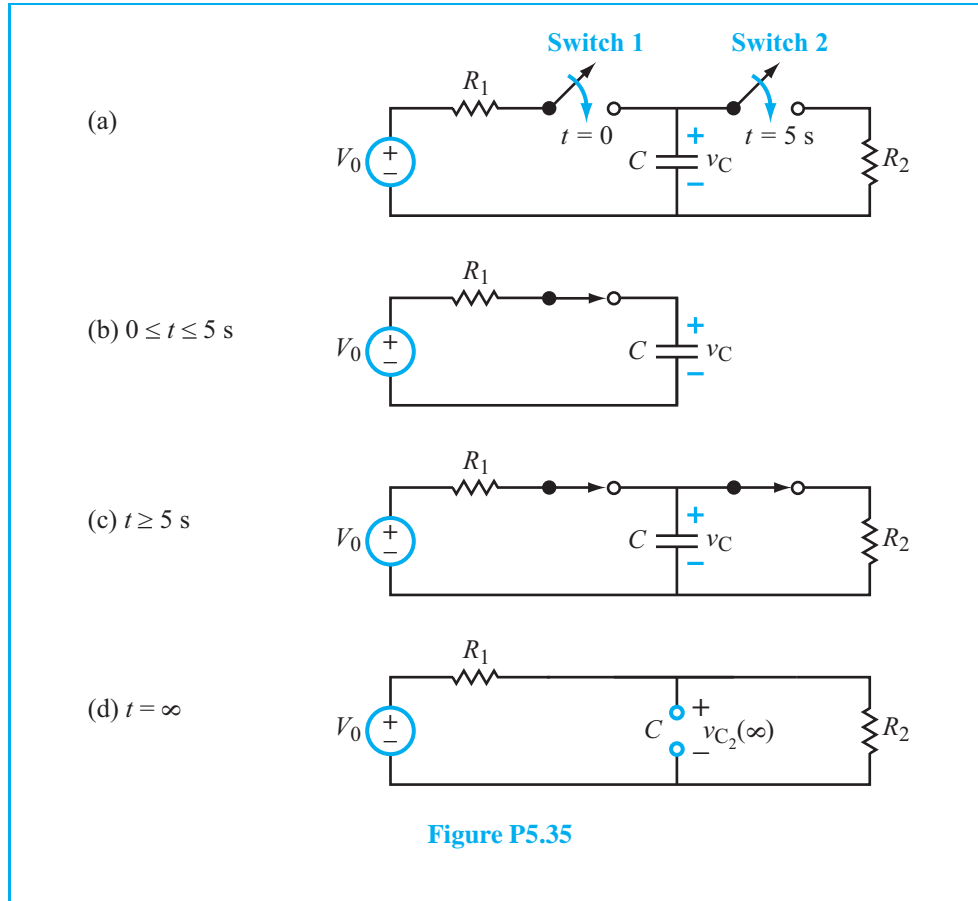


Figure P5.35

**Time Segment 1:  $0 \leq t \leq 5$  s**

$$\begin{aligned}\tau_1 &= R_1 C = 16 \times 10^3 \times 250 \times 10^{-6} = 4 \text{ s.} \\ v_{C_1}(t) &= v_{C_1}(\infty) + (v_{C_1}(0) - v_{C_1}(\infty))e^{-t/\tau_1} \\ &= V_0 + (0 - V_0)e^{-0.25t} \\ &= 24(1 - e^{-0.25t}), \quad \text{for } 0 \leq t \leq 5 \text{ s.}\end{aligned}$$

**Time Segment 2:  $t \geq 5$  s**

Through source transformation, it is easy to see that  $R_1$  and  $R_2$  should be combined in parallel. Hence:

$$\begin{aligned}\tau_2 &= \left( \frac{R_1 R_2}{R_1 + R_2} \right) C = 8 \times 10^3 \times 250 \times 10^{-6} = 2 \text{ s.} \\ v_{C_2}(t) &= v_{C_2}(\infty) + [v_{C_2}(5 \text{ s}) - v_{C_2}(\infty)]e^{-(t-5)/\tau_2}\end{aligned}$$

$$v_{C_2}(\infty) = \frac{V_0 R_2}{R_1 + R_2} = \frac{24 \times 16}{16 + 16} = 12 \text{ V.}$$

$$v_{C_2}(5 \text{ s}) = v_{C_1}(5 \text{ s}) = 24(1 - e^{-0.25 \times 5}) = 17.12 \text{ V}$$

$$\begin{aligned} v_{C_2}(t) &= 12 + [17.12 - 12]e^{-0.5(t-5)} \\ &= 12 + 5.12e^{-0.5(t-5)}, \quad \text{for } t \geq 5 \text{ s.} \end{aligned}$$

Plot is shown in Fig. P5.35(e).

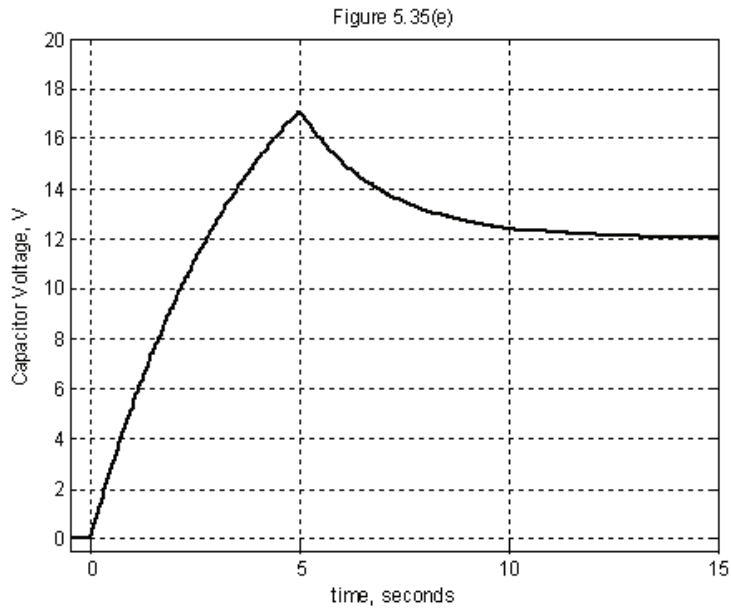



Figure P5.35(e)



## Section 5-4: Response of the RC Circuit

**Problem 5.33** After having been in position 1 for a long time, the switch in the circuit of Fig. P5.33 was moved to position 2 at  $t = 0$ . Given that  $V_0 = 12$  V,  $R_1 = 30$  k $\Omega$ ,  $R_2 = 120$  k $\Omega$ ,  $R_3 = 60$  k $\Omega$ , and  $C = 100$   $\mu$ F, determine:

- (a)  $i_C(0^-)$  and  $v_C(0^-)$
- (b)  $i_C(0)$  and  $v_C(0)$
- (c)  $i_C(\infty)$  and  $v_C(\infty)$
- (d)  $v_C(t)$  for  $t \geq 0$
- (e)  $i_C(t)$  for  $t \geq 0$

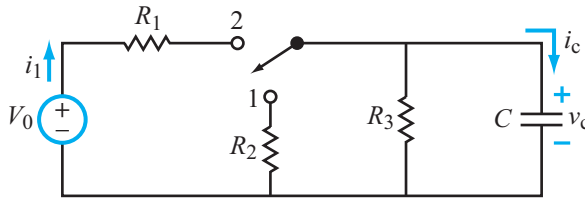

**Figure P5.33:** Circuit for Problem 5.33.


**Solution:** (a) Since the capacitor had access to resistors  $R_2$  and  $R_3$  prior to  $t = 0$ , it has dissipated any charge it may have had, long before  $t = 0$ . Hence,

$$i_C(0^-) = v_C(0^-) = 0.$$

(b) At  $t = 0$ , the capacitor acts like a short circuit (because its voltage cannot change instantaneously). Since the voltage across  $R_3$  is zero, no current flows through it. Hence,


$$i_1(0) = \frac{V_0}{R_1} = \frac{12}{30\text{k}} = 0.4 \text{ mA}.$$

$$v_C(0) = v_C(0^-) = 0.$$

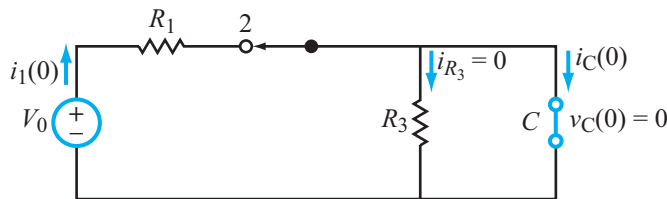

At  $t = 0$

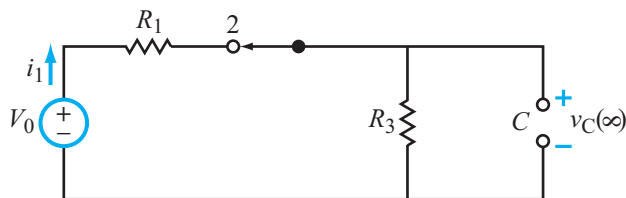(c) At  $t = \infty$ , capacitor acts like an open circuit.



At  $t = \infty$

Hence,

$$i_C(\infty) = 0$$
$$v_C(\infty) = \frac{V_0 R_3}{R_1 + R_3} = \frac{12 \times 60}{30 + 60} = 8 \text{ V}.$$

(d)

$$v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty))e^{-t/\tau}$$
$$= 8 + (0 - 8)e^{-t/\tau}$$
$$= 8(1 - e^{-t/\tau}) \quad (\text{V}), \quad \text{for } t \geq 0,$$

where


$$\tau = \left( \frac{R_1 R_3}{R_1 + R_3} \right) C = \frac{30 \times 60}{30 + 60} \times 10^3 \times 10^{-4} = 2 \text{ s}.$$

(e)

$$i_C(t) = C \frac{dv_C}{dt}$$
$$= 10^{-4} \frac{d}{dt} [8(1 - e^{-0.5t})]$$
$$= 0.4e^{-0.5t} \quad (\text{mA}) \quad \text{for } t \geq 0.$$

**Problem 5.39** The switch in the circuit of Fig. P5.39 had been in position 1 for a long time until it was moved to position 2 at  $t = 0$ . Determine  $v(t)$  for  $t \geq 0$ , given that  $I_0 = 6 \text{ mA}$ ,  $V_0 = 18 \text{ V}$ ,  $R_1 = R_2 = 4 \text{ k}\Omega$ , and  $C = 200 \text{ }\mu\text{F}$ .

**Solution:**

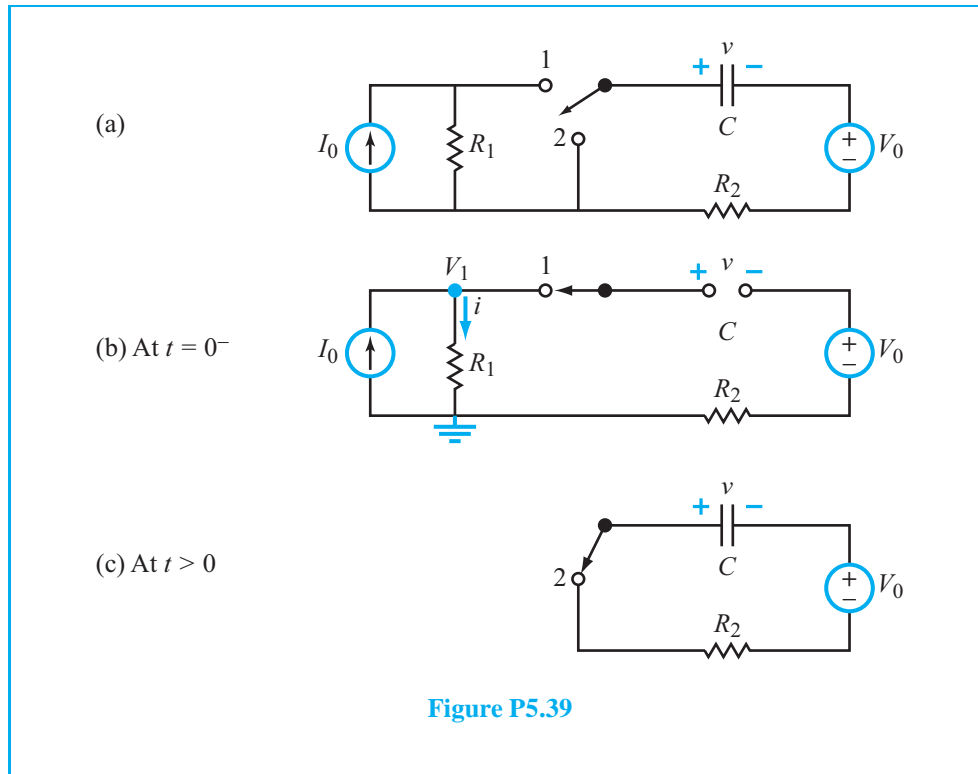

At  $t = 0^-$ , the circuit assumes the condition shown in Fig. 5.39(b).

$$V_1 = I_0 R_1 = 6 \times 10^{-3} \times 4 \times 10^3 = 24 \text{ V.}$$

$$v(0^-) = V_1 - V_0 = 24 - 18 = 6 \text{ V.}$$

At  $t > 0$ , circuit becomes as shown in Fig. P5.39(c). Now,

$$v(\infty) = -V_0 = -18 \text{ V.}$$

$$\tau = R_2 C = 4 \times 10^3 \times 2 \times 10^{-4} = 0.8 \text{ s.}$$

Hence,

$$\begin{aligned} v(t) &= [v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}] \\ &= [-18 + [6 + 18]e^{-1.25t}] \\ &= [-18 + 24e^{-1.25t}] \quad (\text{V}), \quad \text{for } t \geq 0. \end{aligned}$$