
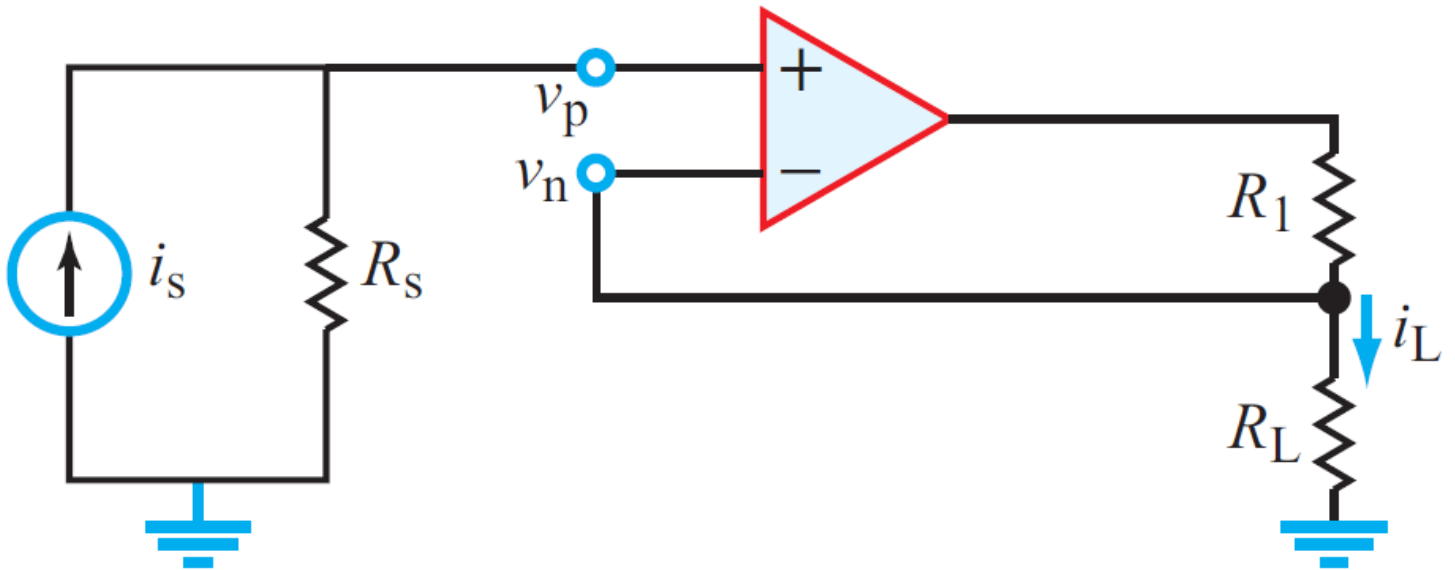


1. For the op-amp circuit shown below:

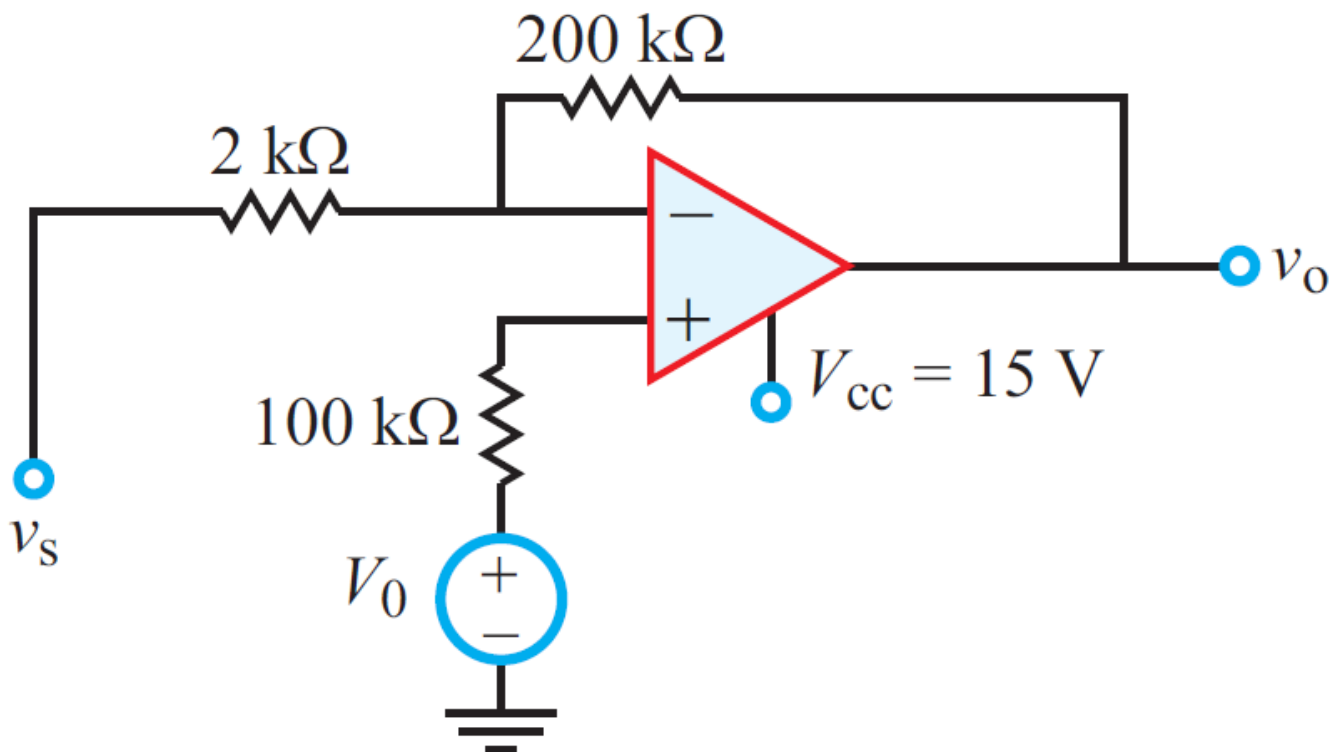


- (a) Use the non-ideal op amp model (Figure 4-4 in the book) to develop an expression for the current gain $G_i = i_L / i_s$.
 (b) Simplify the expression by assuming $A \rightarrow \infty$, $R_i \rightarrow \infty$, and $R_o \rightarrow 0$.


2. Determine the output voltage for the circuit below and specify the linear range for v_s , given that $V_{cc} = 15\text{ V}$ and $V_0 = 0$.



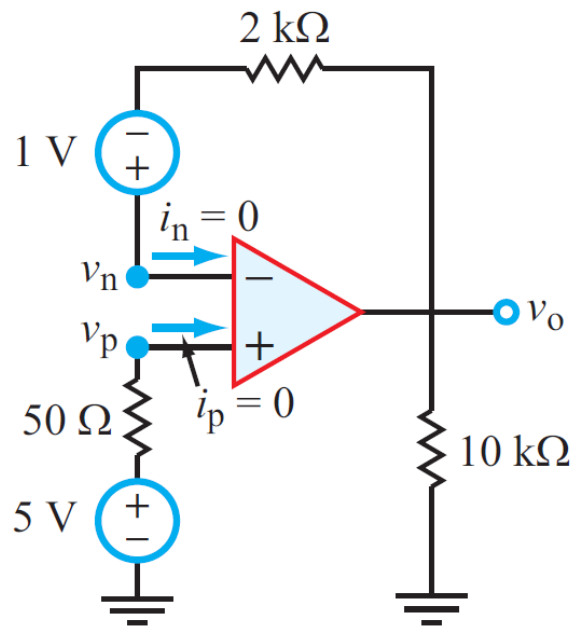3. Determine v_o across the 10-k Ω resistor in the circuit below.



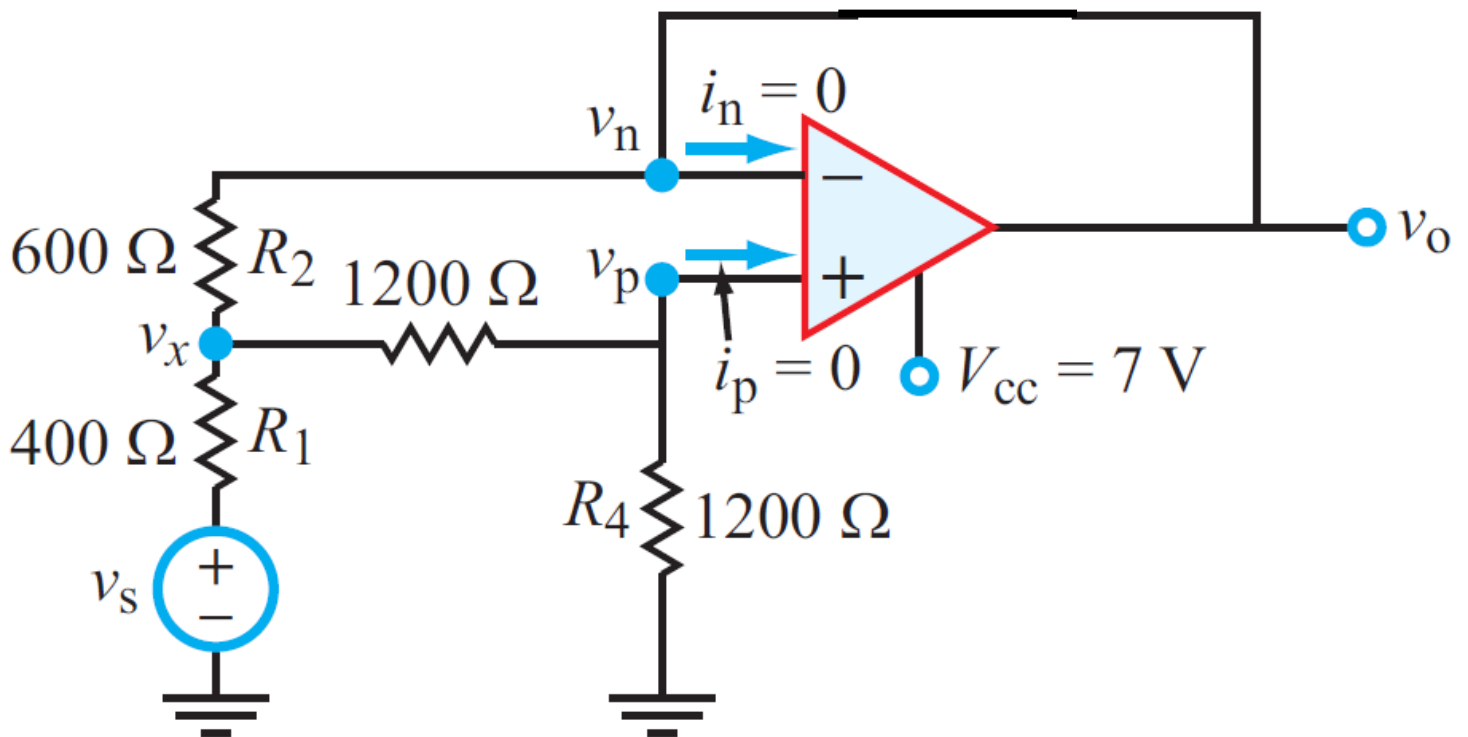4. Evaluate $G = v_o/v_s$ for the circuit below AND specify the linear range of v_s .



5. In the circuit below, op amp 1 receives feedback at its input from its own output as well as from the output of op amp 2. Relate v_o to v_s .

