
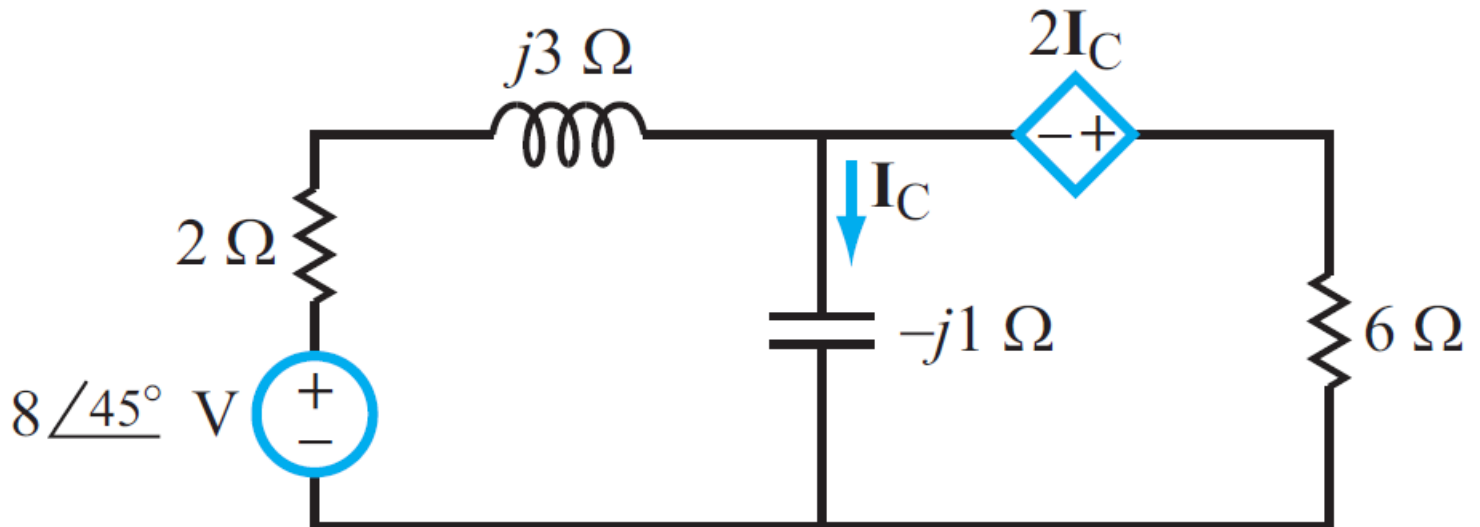


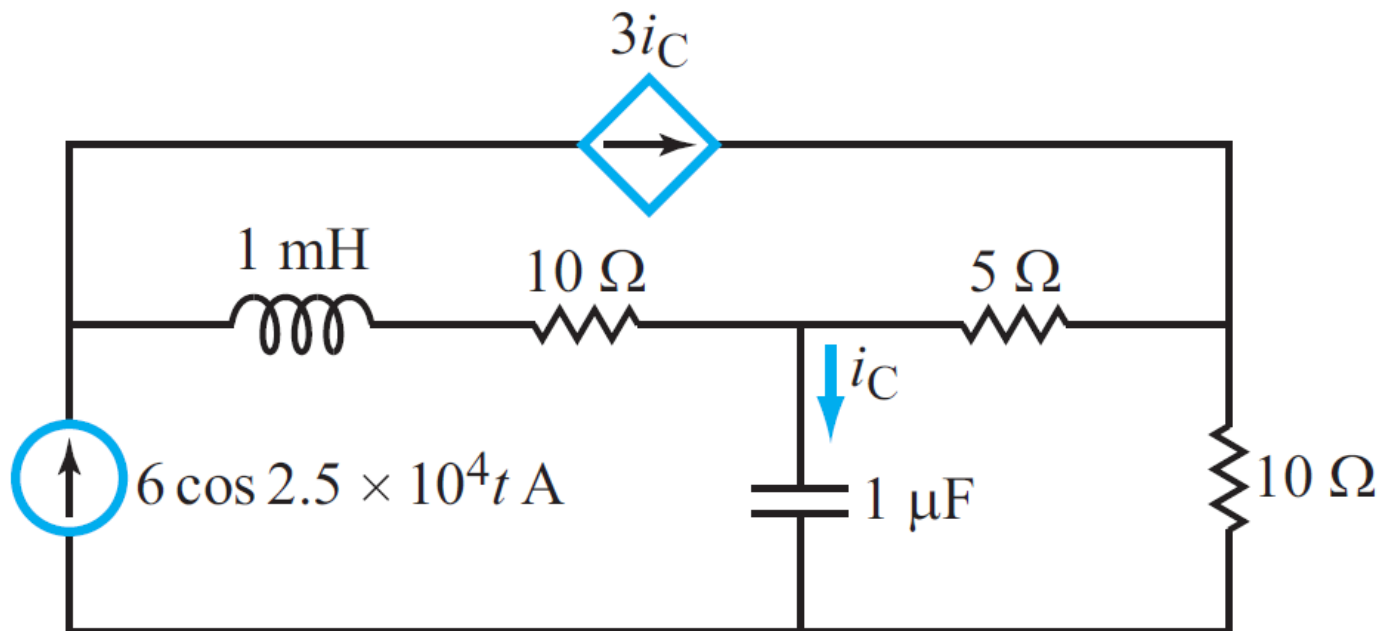
1. Apply nodal analysis to determine I_C in the circuit below.




2. Use any analysis technique of your choice to determine $i_C(t)$ in the circuit below.



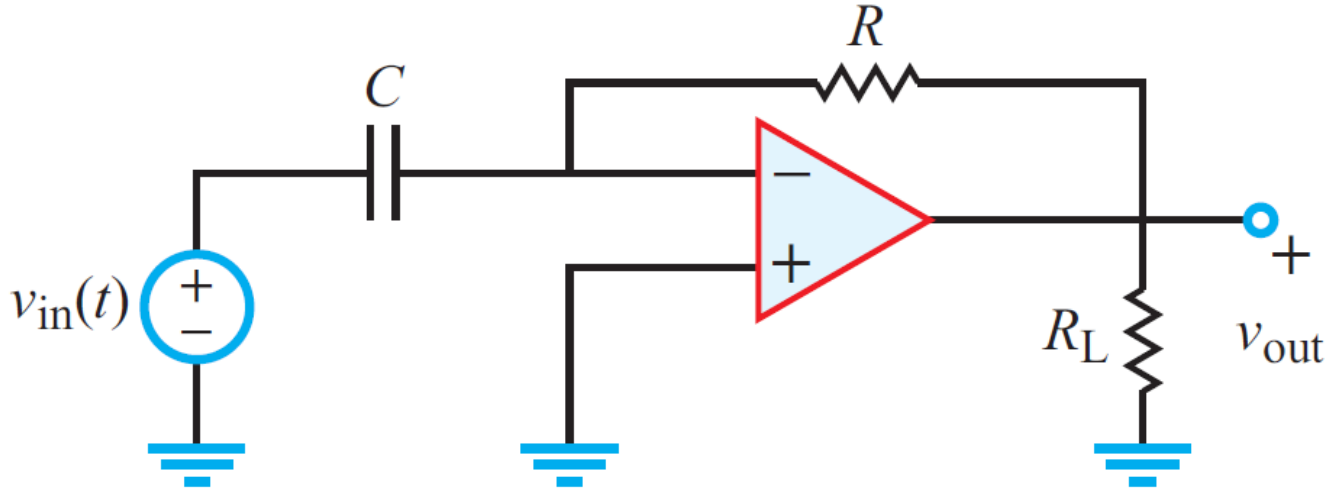3. The input signal in the op-amp circuit below is given by $v_{in}(t) = V_0 \cos \omega t$. Assuming the op amp is operating within its linear range, obtain an expression for $v_{out}(t)$ by applying the phasor-domain technique, and then evaluate it for the frequency at which $\omega RC = 1$.



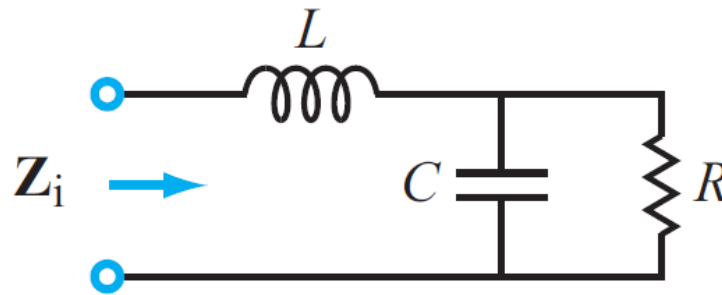4. Determine the resonant frequency of the circuit below, given that $R = 100 \, \Omega$, $L = 5 \, \text{mH}$, and $C = 1 \, \mu\text{F}$.



5. For the two circuits shown below, determine

(a) the transfer function $\mathbf{H} = \mathbf{V}_o / \mathbf{V}_i$

(b) the frequency ω_0 at which \mathbf{H} is purely real.

