

YOUR NAME:

YOUR SID:

YOUR PARTNER'S NAME:

YOUR PARTNER'S SID:

Pre-Lab: ____/50

Lab: ____/50

Total: ____/100

Resistive Circuits

Lab 2: Resistive Circuits

ELECTRICAL ENGINEERING 40

INTRODUCTION TO MICROELECTRONIC CIRCUITS

Department of Electrical Engineering and Computer Sciences

Professor Michel Maharbiz, Vincent Lee, Linda Dai, Hiroko Kawana

Lab Contents

- I. Lab Objectives
- II. Pre-Lab: Introducing Multisim! And other stuff...
 - a. Pre-Lab Assignment
 - b. Resistor Color Codes
- III. Lab Section
 - a. A Word of Caution
 - b. Lab Equipment: Digital Multimeter (DMM), Power Supply, and Solderless Protoboards
 - i. The Digital Multimeter
 - ii. The Programmable Power Supply
 - iii. Solderless Protoboard (Breadboard)
 - c. Resistive Networks
 - d. Resistor Voltage Divider
- IV. Lab Submissions
 - a. Image Citations

Lab Objectives

The pre-lab portion of this lab is intended to get you acquainted with the basics of circuit CAD (**Computer Aided Design**) software. We will be using Multisim as our primary tool to design and simulate the circuits we will build in the lab.

The lab is intended to introduce you to basic electrical components, and to help you become familiar with electronic equipment that you will use to design, build, and test circuits. In this lab, we will start by analyzing resistive circuits, and then later analyzing potentiometers.

There is no post-lab section for this lab or any of the following labs, however you are expected to complete all questions in these documents and turn it in as your lab report. You have one section to complete this lab. These labs must be completed in **pairs**, but only one lab report per team is required. When you make measurements, where appropriate, please use at least 2 to 3 decimal places and include units.

Pre-Lab: Introducing Multisim! and other stuff.

Multisim is a circuit CAD software where you can virtually prototype most of your circuits. It is a great tool that simulates your circuit, allowing you to check whether or not the schematic you drafted will work in practice.

Simulating a prototype before building the actual circuit will save hours of debugging in the lab. (We're going to warn you now; debugging your circuit in lab is probably more frustrating than a segmentation fault in CS61C).

To minimize the amount of time you spending spinning your wheels, we will first simulate our circuits in Multisim's simulation environment, and then build it when you arrive in the lab. Therefore, it is essential that before each lab, that you actually design and simulate your circuit in the simulator **BEFORE** coming to lab (otherwise you will NOT finish in the allotted three hours).

As part of your pre-lab assignment, we will be referring to the textbook to get a jump start with Multisim.

Pre-Lab Assignment

1. Read section 2-8 (pg. 66-72) in the Circuits textbook written by your immodest instructor 😊.
2. Simulate the circuits shown in Figures 2-40, 2-41, 2-42, 2-43, and 2-44. Save these somewhere so that you can access them in the lab and **attach a print out** of each circuit to the end of this lab. The lab machines have Multisim installed on them. **(5 circuits x 4 pts each)**
3. Complete Exercises 2-17 and 2-18 and **attach them** to this lab. **(2 exercises x 10 pts each)**
4. Read the following section on Resistor Color Codes and complete the exercises.
5. Familiarize yourself with the rest of this document before arriving in lab!

In addition, we recommend that you take a look at some documentation to learn the basics before you get started. Below are also links to some useful tutorials...

The User's Manual for Multisim can be found [here](#)

The Getting Started Guide can be found [here](#)

Resistor Codes

In every lab we will be using a lot of resistors, specifically many resistors of different values. So, how do we tell resistors apart?

Every resistor has a series of color markings or bands that indicate the value of the resistor by the resistor color code. For most resistors, three closely-spaced color bands are followed by a fourth color band. The first two bands represent the first two significant figures of the resistor value, the third band corresponds to the multiplier as a power of ten, and the fourth band determines the resistor tolerance as a measure of possible resistor values within a certain range. Occasionally, there is a fifth band that indicates the quality in terms of the percentage of resistors that fail every 1000 hours.

To calculate the value of the resistor, we interpret these color codes by using the following equation:

$$ab \times 10^c \text{ Ohms}$$

where

- a = the number corresponding to the first color band
- b = the number corresponding to the second color band
- c = the number corresponding to the third color band

Below is a table of corresponding numbers to each color in the resistor:

Black	Brown	Red	Orange	Yellow	Green	Blue	Violet	Grey	White
0	1	2	3	4	5	6	7	8	9

Ask your local circuits GSI if you need a mnemonic to remember this...

For example, in Figure 1 we have the color band sequence blue-grey-brown-gold, which is read in that order. The blue band corresponds to 6 and the grey band corresponds to 8, which gives us 68. Combining this with the multiplier value of 1, we get $68 \times 10^1 = 680 \text{ Ohms}$. The gold band corresponds to 5% tolerance, so the value of the resistor falls within the range $[680 - .05(680)]\Omega$ and $[680 + .05(680)]\Omega$.



Figure 1ⁱ



Figure 2ⁱⁱ

Now it's your turn, given the color band sequence orange-orange-red-gold in Figure 2, what is the value of this resistor R? (Make sure to include units!)

R = (4 pts)

Given that the resistor tolerance band gold corresponds to 5% tolerance, what are the largest and smallest values this resistor can have (**3 pts each**)? (Ideally if the manufacturer did a good job, every resistor would be manufactured to have the same value).

Largest value = Smallest value =

Public Service Announcement: PLEASE RETURN YOUR RESISTORS TO THE CORRECT BIN AFTER YOU FINISH THE LAB. IF YOU DON'T BAD THINGS MAY HAPPEN 😊

Lab Section

In our labs we will be working with electronic equipment to supply. Before proceeding with the rest of this lab, please read the next section carefully...

A Word of Caution



In these labs you will be working with electronic equipment, which supply power to your circuits. The labs in this course are designed to operate on voltages less than 25V. These voltages level are not harmful and do not deliver sufficient energy to cause bodily harm (the resistance of your body is on the order of 300 to 1000 *Ohms*). However, the equipment we are using is capable of generating higher voltages, which is powered by the high household power grid operating at 110 to 240V. **This can potentially be harmful.**

Another hazard in these labs is hot circuit components. At one point or another in these labs, you may connect something incorrectly and the component may get really hot. **Be careful not to get burned!**

To avoid these hazards we highly recommend exercising the following precautions when working in the lab:

1. Turn off all power supplies when modifying a laboratory setup or performing manipulations that could potentially expose you to high voltageⁱⁱⁱ.
2. Set a current and voltage limit on any power supplies you use. We will discuss this later in the lab, but for now, be aware that a current and voltage limit prevent electrical risks and protect your IC from going up in smoke.
3. Exercise extreme caution before touching a laboratory setup. Can you feel heat radiating from you circuit component? Consult your lab GSI if you're not sure^{iv}.



Lab Equipment: Digital Multimeter (DMM), Power Supply, and Solderless Protoboards

All electronic gadgets need power to operate (or else they wouldn't be "electronic"). Most systems require a specific supply voltage in order for the device to operate. For example, the "power brick" for a conventional laptop must supply 20V. You can usually find operating voltages on the labels of your electronic devices.

Generally, power supplies and digital multimeters are the most common tools used for powering circuits and ensuring that circuits are functioning correctly. We will be using these tools for the majority of our labs. Download and read the instructions from the course web on how to operate the programmable laboratory supply and the digital multimeter. The link to the instructions can be found [here](#).

If you still do not understand how to operate the equipment, download the user's manual or consult your lab GSI.

The Digital Multimeter (DMM)



Agilent DMM 34401A^v

The digital multimeter measures a number of different quantities, from capacitance and resistance, to frequency. In this lab, we are most interested in voltage and current. We will use the DMM not only to check the output of the circuits we design, but also to verify our setup.

Some of the questions you should consider when using the DMM are:

Does the voltage supplied to the circuit have the correct value?

Is the supply current in the expected range (i.e. not something like 10kAmps)?

Performing sanity checks like these will make your life much easier in the lab.

The Programmable Power Supply


In many applications, electronic equipment is powered by batteries. However, prototyping circuits that are battery powered is problematic because discharged batteries are always a hazard. The power supply eliminates this problem.

Agilent E3631 Programmable Power Supply^{vi}

The programmable power supply also helps us avoid inconsistencies in powering our circuits by delivering a constant voltage, which you can set by changing the output voltage.

Most laboratory supplies also have a current limit feature that you can use to set the maximum current the supply will deliver regardless of what voltage you specify.

Why should we set the current limit?

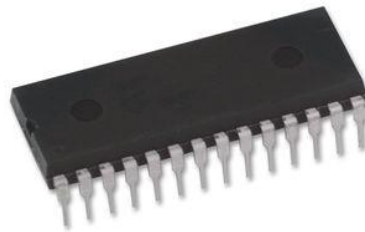Your new IC chip^{vii}

Suppose you are testing a new circuit with your brand new \$1 million chip. You expect your new chip to nominally draw 100mA . But unfortunately for you, you wired something wrong and instead of drawing 100mA your chip draws 1kA (10^5 times what you expected it to draw!).

Your basic physics class in high school taught you that power is proportional to voltage times current ($P = IV$). Even if voltage is set at 1V , your brand new \$1 million chip has dissipated a lot of power in the form of wasted heat. Now, your brand new \$1 million chip is fried or your programmable power supply needs a new fuse.

The current limit is designed to prevent exactly this. The current limit will prevent the output current from exceeding a certain value so that excessive current flow will not destroy your setup. We usually set the current limit at a small margin above nominal draw. (Usually 100mA to 200mA is usually a good start).

Now for a few quick questions...

Suppose you have designed a new audio amplifier and are now ready to test it in the laboratory. According to the design, the circuit can be modeled as a $1k\Omega$ resistor and we need to apply a voltage V_{dd} across it. To ensure that your circuit does not go up in smoke like the \$1 million chip in the previous example, we set the current limit to I_{max} . For the following values of V_{dd} and I_{max} what voltage and current will your power supply **actually** provide in this set up? (Hint: given the resistance, determine if the circuit draws more current than the current limit)

Let $V_{dd} = 5V$ and $I_{max} = 10mA$ as your values.

(1 pt each)


What if $V_{dd} = 10V$ and $I_{max} = 5mA$ as your values?

(1 pt each)

Solderless Protoboards (Breadboards)

In the following exercises, you will be using the solderless protoboard, known affectionately as the breadboard.

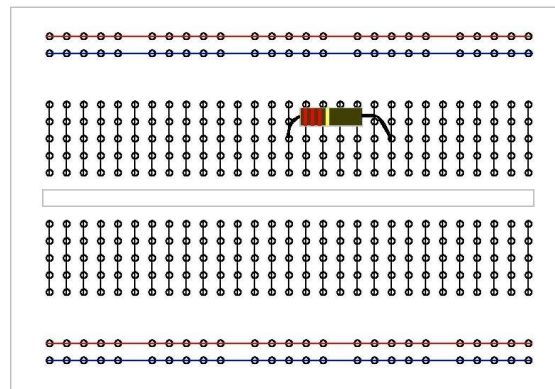The breadboard is a convenient set of traces that help you prototype your circuit by providing sets of pre-made connections. A series of wire or metal contacts within the breadboard allow current and voltage to flow through the prototyped circuit. The figure below indicates which holes on the breadboard are connected.



A typical breadboard and its traces^{viii}


Notice that the breadboard at your station looks slightly different but the connections follow the same pattern. Also note that there are designated banana plug connectors on the breadboard. Be aware that these connectors do not connect to any other part of the board by themselves. In order to use the banana plug connectors, you have to wire them to appropriate traces on the board.

Also notice the red and blue traces are longer than the traces in the middle of the board. These red and blue traces are usually designated as power traces there you should hook up your positive, and negative supplies. It is strongly recommended that you connect your supplies to you power traces as opposed to some random trace on the breadboard so that it allow convenient access and organization to the supplies and ground connections.

Resistive Networks

Now let's move on to something you did in the pre-lab.

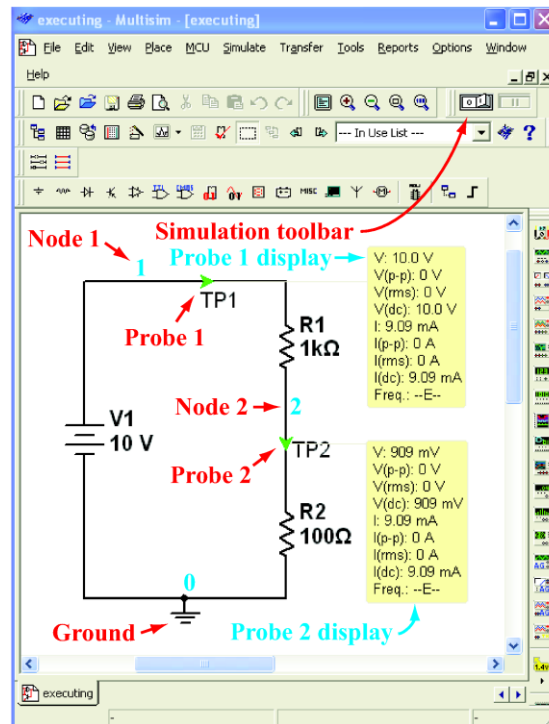Your first task will be to build the circuit you simulated in the pre-lab. Open up the file for the circuit you simulated in Figure 2-41 and build it on the protoboard.



Executing a simulation¹

Using the DMM, measure the value of the voltage at Node 2 of the circuit and compare it to the value you get in the simulation. If you don't know how to connect the DMM correctly, ask your GSI for help.

By now you should have read off some values from your simulator as to what the voltage is at each node of each of the circuits. In the space provided below, record your voltage measurements for Node 2. It should not match the simulator value exactly. Explain why this is the case.

Score: __/4

¹ Ulaby and Maharbiz. Circuits, Figure 2-41

Now let's examine the behavior of resistors. You already have learned that when we put resistors in series the equivalent resistance R_{eq} of a series of n resistors is equal to:

$$R_{eq} = \sum_{i=1}^n R_i \quad \text{Equivalent Resistance in Series}$$

Combining In-Series Resistors

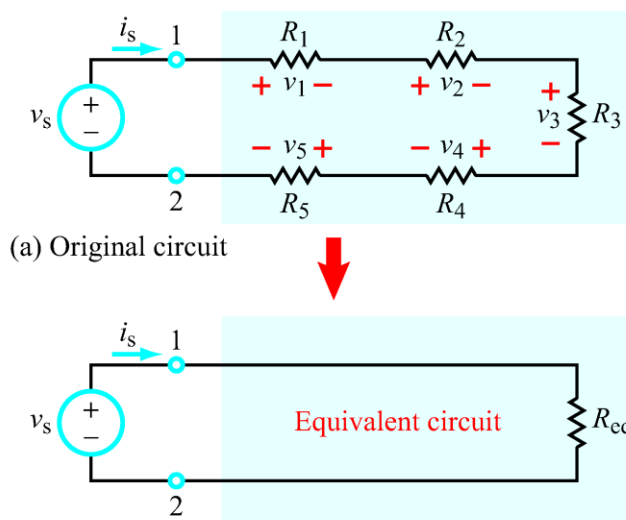


Figure 2-17: In a single-loop circuit, R_{eq} is equal to the sum of the resistors.²

And for a network of n parallel resistors, the equivalent resistance R_{eq} is equal to:

$$R_{eq} = \left(\sum_{i=1}^n \frac{1}{R_i} \right)^{-1} \quad \text{Equivalent Resistance in Parallel}$$

In a relatively simple resistive network, we can use these rules to implement another rule: the voltage divider. The voltage divider equation allows you to calculate the voltage across certain resistor configurations

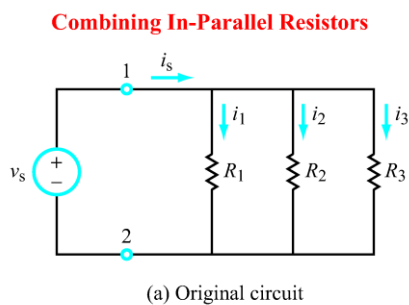



Figure 2-21: Voltage source connected to a parallel combination of three resistors.³

Resistor Voltage Divider

Sometimes you just can't get you what you need to power your device properly. You have a 9V battery but your circuit runs on 2 AA batteries (3V). So what do you do?

A rather primitive solution is to use a voltage divider to step down a higher voltage to a lower one. Suppose we have a voltage source V_S and we want to use that to deliver a certain voltage V_L to a device (assume $V_L < V_S$). In addition, we want to accomplish this using only resistors and the voltage source using voltage division. Let's do some calculations to figure out what resistor values to use.

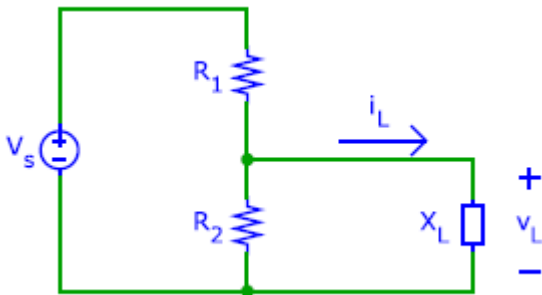The circuit in consideration looks like the following:



The resistance X_L of a practical load (the device) will vary, so we will not be able to get the exact desired load voltage at all times. Instead, we will compromise with an acceptable range for V_L .


Suppose that V_L must stay between $V_{L,\min}$ and $V_{L,\max}$ as the load current i_L is varied between zero and $i_{L,\max}$. Then the allowable change in V_L is $\Delta V_L = V_{L,\max} - V_{L,\min}$.

In addition, we want to minimize the amount of power dissipated by R_1 and R_2 in order to maximize the efficiency

of the circuit.

Considering these constraints, we want to solve for optimal R_1 and R_2 in terms of V_S , $V_{L,\max}$, ΔV_L , and $i_{L,\max}$.

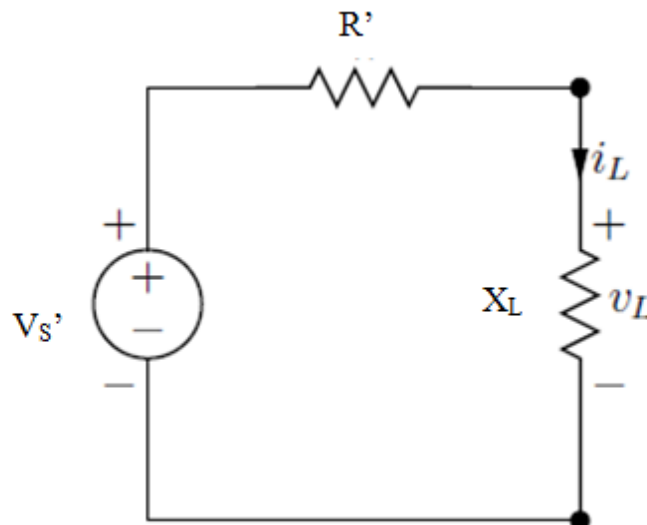It is easier to calculate by first expressing the above circuit as this equivalent circuit:



³ Ulaby and Maharbiz. Circuits, Figure 2-21

Show that the follow relationships hold (hint: think about what happens when $X_L=0$ and $X_L=\infty$):

$$V_S' = V_S \frac{R_2}{R_1 + R_2}$$

$$R' = \frac{R_1 R_2}{R_1 + R_2}$$

Score: _ / 4

By looking at the equivalent circuit we see that we need to achieve a balance: we want R' to be small enough so that ΔV_L is small, but we also want R' to be as large as possible to minimize the power consumed by the divider.

1. The highest output voltage $V_{L,\max}$ occurs when $X_L \rightarrow \infty$, in other words, when the load acts like a open circuit. What is $V_{L,\max}$ in terms of V_S' and R' ?

_____ (2 pt)

2. $V_{L,\min}$ occurs when $i_L = i_{L,\max}$. Express $V_{L,\min}$ in terms of V_S' , R' , and $i_{L,\max}$.

_____ (2 pt)

3. Find ΔV_L from parts 1 and 2.

_____ (2 pt)

4. Find the power consumed (wasted) by R_1 and R_2 when $i_L = i_{L,\max}$ in terms of V_S , R_1 , R_2 , and $V_{L,\min}$

_____ (2pt)

5. Calculate the efficiency (power delivered to the load divided by total power) when $i_L = i_{L,\max}$ in terms of V_S , R_1 , R_2 , $V_{L,\min}$, and $i_{L,\max}$.

_____ (2pt)

Solve the equations from parts 1 and 3 simultaneously to find R_1 and R_2 in terms of V_S , $V_{L,\max}$, ΔV_L , and $i_{L,\max}$.

Score: _ / 6

$R_1 =$


$R_2 =$

Now that you've derived the formulas for the resistances satisfying the parameters, let's actually build the circuit.

Supposed we want to use our circuit to step down a supply voltage of $V_s = 9V$ to power a load with that requires a supply voltage $V_L = 3V \pm 25\%$ to operate. We also want the maximum current running through the load to be $i_{max} = 10mA$.

What are values of R_1 and R_2 should you use? **(1 pts each)**

$R_1 =$ $R_2 =$

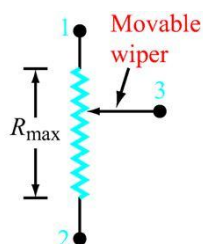

(b) Potentiometer

For our prototype we will be using a variable resistor or a potentiometer to change the load to the circuit. The symbol for a potentiometer is shown in the figure to the left.⁴

To simulate the variable load, we will be connecting the A and W terminals of the potentiometer as our X_L load.


Once you have built your circuit, adjust the potentiometer and verify that the output voltage across the load stays within the range specified by the parameters.

For loads close to zero, obviously we will not be able to satisfy the parameters so don't worry about those loads when you adjust the potentiometer.

The potentiometer has three pins. The two outer pins will always have the same resistance across them. The resistance between the middle and each of the outer pins will vary as you turn the knob. Finally, the resistance between the first outer pin and the middle pin, plus the resistance of the second outer pin and the middle pin, should add up to the resistance between the two outer pins at all times.

Show this set up to your GSI for check off.

Your GSI Signs Here **(20 pts)**

 

⁴Ulaby and Maharbiz. Circuits, Figure 2-3 (b)

Lab Report Submissions

This lab is due **at the beginning** of the next lab section. Make sure you have **completed all questions** and **drawn all the diagrams** for this lab. In addition, attach any loose papers specified by the lab and submit them with this document.

These labs are designed to be completed in **groups of two**. Only one person in your team is required to submit the lab report. Make sure the names and student IDs of **BOTH** team members are on this document (preferably on the front).

Image Citations

Textbook Images are courtesy of Fawwaz T. Ulaby and Michel M. Maharbiz and National Technology and Science Press.

Fawwaz T. Ulaby and Michel M. Maharbiz, Circuits © 2009 National Technology and Science Press

Additional Citations

-
- i www.parts.digikey.es
 - ii www.ca.digikey.com
 - iii www.constructionstore.co.uk
 - iv www.speedysigns.com
 - v home.agilent.com
 - vi www.triosmartcal.com.au
 - vii www.octopart.com
 - viii www.engr.astate.edu