

Problem 1.13 A steady flow resulted in 3×10^{15} electrons entering a device in 0.1 ms. What is the current?

Solution:

$$i = \frac{\Delta Q}{\Delta t} = \frac{n_e e}{\Delta t} = \frac{3 \times 10^{15} \times 1.6 \times 10^{-19}}{0.1 \times 10^{-3}} = 4.8 \text{ A}.$$

Problem 2.14 Determine currents I_1 to I_3 in the circuit of Fig. P2.14.

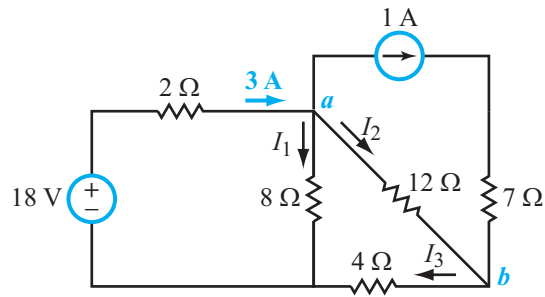


Figure P2.14: Circuit for Problem 2.14.

Solution: For the loop containing the 18-V source,

$$-18 + 3 \times 2 + 8I_1 = 0.$$

Hence, $I_1 = 1.5$ A.

KCL at node a gives

$$3 - 1 - I_1 - I_2 = 0$$

$$I_2 = 2 - I_1 = 2 - 1.5 = 0.5 \text{ A.}$$

KCL at node b gives

$$1 + I_2 - I_3 = 0$$

$$I_3 = 1 + I_2 = 1 + 0.5 = 1.5 \text{ A.}$$

Problem 1.15 The plot in Fig. P1.15 displays the cumulative amount of charge $q(t)$ that has entered a certain device up to time t . What is the current at

- (a) $t = 1$ s
- (b) $t = 3$ s
- (c) $t = 6$ s

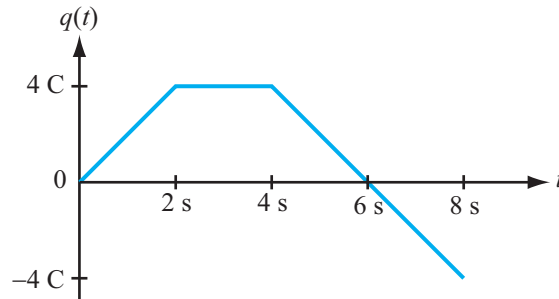


Figure P1.15: $q(t)$ for Problem 1.15.

Solution:

- (a) $i = \frac{4}{2} = 2$ A @ $t = 1$ s (slope of first segment).
- (b) $i = 0$ @ $t = 3$ s (slope of $q(t) = 0$ at $t = 3$ s).
- (c) $i = \frac{-4}{2} = -2$ A @ $t = 6$ s (negative slope of third segment).

Problem 2.15 Determine I_x in the circuit of Fig. P2.15.

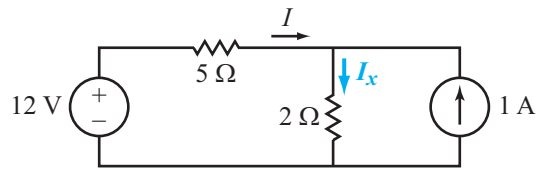


Figure P2.15: Circuit for Problem 2.15.

Solution:

KVL gives: $-12 + 5I + 2I_x = 0$.

KCL gives: $I + 1 - I_x = 0$.

Solution of the two equations yields $I_x = \frac{17}{7} = 2.43$ A.

Problem 2.16 Determine currents I_1 to I_4 in the circuit of Fig. P2.16.

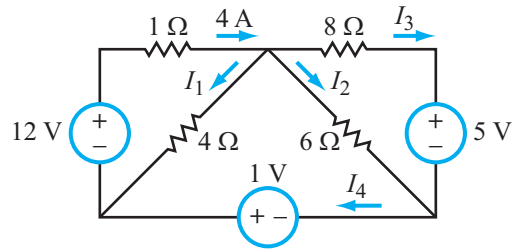


Figure P2.16: Circuit for Problem 2.16.

Solution: Application of KVL to the outer-parameter loop gives

$$-12 + 4 \times 1 + 8I_3 + 5 - 1 = 0,$$

which gives

$$I_3 = 0.5 \text{ A.}$$

KVL for the left-most loop is

$$-12 + 4 \times 1 + 4I_1 = 0,$$

which leads to

$$I_1 = 2 \text{ A.}$$

KCL at the top center node gives

$$4 - I_1 - I_2 - I_3 = 0$$

or

$$I_2 = 4 - I_1 - I_3 = 4 - 2 - 0.5 = 1.5 \text{ A.}$$

KCL at the bottom left node gives

$$I_4 + I_1 - 4 = 0,$$

or

$$I_4 = 4 - I_1 = 4 - 2 = 2 \text{ A.}$$

Sections 1-4 and 1-5: Voltage, Power, and Circuit Elements

Problem 1.17 For each of the eight devices in the circuit of Fig. P1.17, determine whether the device is a supplier or a recipient of power and how much power it is supplying or receiving.

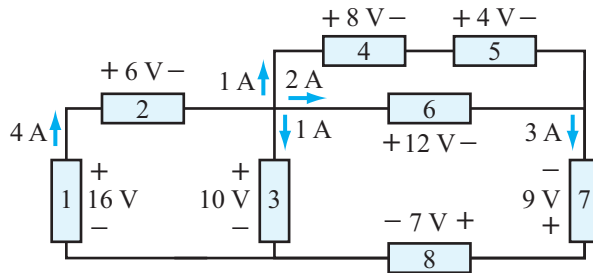


Figure P1.17: Circuit for Problem 1.17.

Solution:

Device 1: $p = vi = 16 \times (-4) = -64 \text{ W}$ (supplier)

Device 2: $p = vi = 6 \times 4 = 24 \text{ W}$ (recipient)

Device 3: $p = vi = 10 \times 1 = 10 \text{ W}$ (recipient)

Device 4: $p = vi = 8 \times 1 = 8 \text{ W}$ (recipient)

Device 5: $p = vi = 4 \times 1 = 4 \text{ W}$ (recipient)

Device 6: $p = vi = 12 \times 4 = 24 \text{ W}$ (recipient)

Device 7: $p = vi = 9 \times (-3) = -27 \text{ W}$ (supplier)

Device 8: $p = vi = 7 \times 3 = 21 \text{ W}$ (recipient)

Problem 1.7 Determine the current $i(t)$ flowing through a resistor if the cumulative charge that has flowed through it up to time t is given by

(a) $q(t) = 3.6t$ mC

(b) $q(t) = 5 \sin(377t)$ μC

(c) $q(t) = 0.3[1 - e^{-0.4t}]$ pC

(d) $q(t) = 0.2t \sin(120\pi t)$ nC

Solution:

(a) $i(t) = \frac{dq}{dt} = \frac{d}{dt}(3.6t \times 10^{-3}) = 3.6 \times 10^{-3} = 3.6$ (mA).

(b) $i(t) = \frac{dq}{dt} = \frac{d}{dt}[(5 \sin 377t) \times 10^{-6}] = 5 \times 377 \times 10^{-6} \cos 377t = 1.885 \cos 377t$ (mA).

(c) $i(t) = \frac{dq}{dt} = \frac{d}{dt}[0.3(1 - e^{-0.4t}) \times 10^{-12}] = 0.3 \times 10^{-12} \times (-0.4) \times (-e^{-0.4t})$
 $= 0.12e^{-0.4t}$ (pA).

(d) $i(t) = \frac{dq}{dt} = \frac{d}{dt}[(0.2t \sin 120\pi t) \times 10^{-9}]$
 $= (0.2 \sin 120\pi t + 0.2t \times 120\pi \cos 120\pi t) \times 10^{-9}$
 $= 0.2 \sin 120\pi t + 75.4t \cos 120\pi t$ (nA).