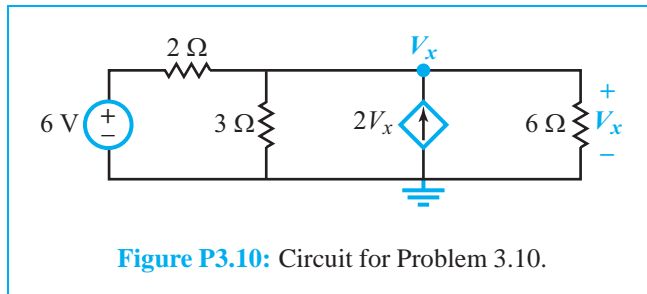


Problem 3.10 The circuit in Fig. P3.10 contains a dependent current source. Determine the voltage V_x .




Solution: In terms of the node voltage V_x , KCL gives

$$\frac{V_x - 6}{2} + \frac{V_x}{3} - 2V_x + \frac{V_x}{6} = 0,$$

whose solution leads to

$$V_x = -3 \text{ V}.$$

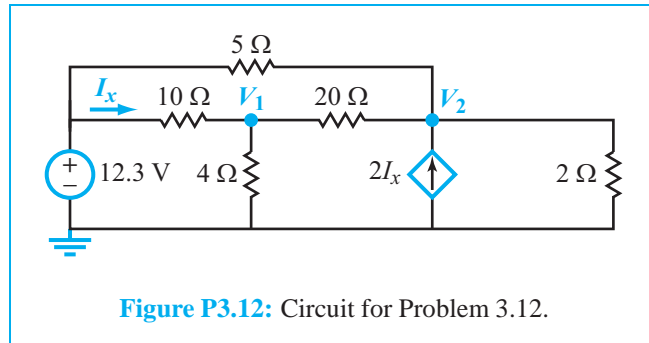Problem 3.12 The magnitude of the dependent current source in the circuit of Fig. P3.12 depends on the current I_x flowing through the $10\text{-}\Omega$ resistor. Determine I_x .



Solution: In terms of the designated node voltages V_1 and V_2 , KCL gives:

$$\text{Node 1: } \frac{V_1 - 12.3}{10} + \frac{V_1}{4} + \frac{V_1 - V_2}{20} = 0 \quad (1)$$

$$\text{Node 2: } \frac{V_2 - V_1}{20} + \frac{V_2 - 12.3}{5} + \frac{V_2}{2} - 2I_x = 0 \quad (2)$$


In addition,

$$I_x = \frac{12.3 - V_1}{10}. \quad (3)$$

Solution of the three equations leads to:

$$V_1 = 3.8 \text{ V}, \quad V_2 = 5.8 \text{ V}, \quad I_x = 0.85 \text{ A}.$$

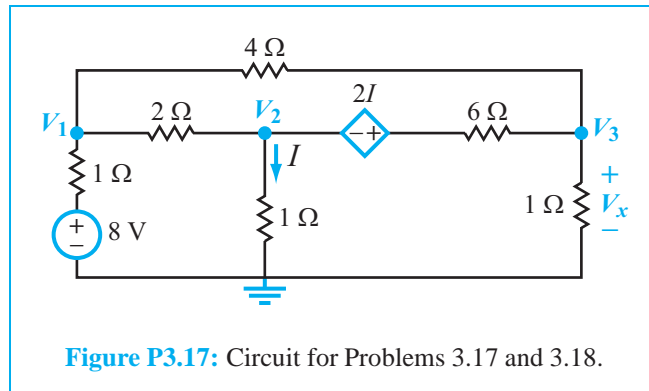Problem 3.17 Determine V_x in the circuit of Fig. P3.17.



Solution: The node equations for designated nodes V_1 , V_2 , and V_3 are:

$$\frac{V_1 - 8}{1} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = 0, \quad (1)$$

$$\frac{V_2 - V_1}{2} + \frac{V_2 + 2I - V_3}{6} + \frac{V_2}{1} = 0, \quad (2)$$

$$\frac{V_3 - 2I - V_2}{6} + \frac{V_3}{1} + \frac{V_3 - V_1}{4} = 0, \quad (3)$$

and the current I is related to V_2 by

$$I = \frac{V_2}{1} = V_2. \quad (4)$$

The solution of the simultaneous equations gives

$$V_1 = 5.18 \text{ V}, \quad V_2 = 1.41 \text{ V}, \quad V_3 = 1.41 \text{ V},$$

and

$$V_x = V_3 = 1.41 \text{ V}.$$

Problem 3.23 Determine V in the circuit of Fig. P3.23 using mesh analysis.

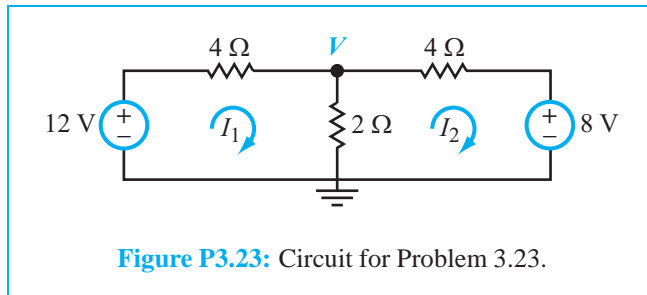


Figure P3.23: Circuit for Problem 3.23.

Solution:

$$\text{Mesh 1:} \quad -12 + 4I_1 + 2(I_1 - I_2) = 0$$

$$\text{Mesh 2:} \quad 2(I_2 - I_1) + 4I_2 + 8 = 0$$

Solution is:

$$I_1 = \frac{28}{16} \text{ A}, \quad I_2 = \frac{-12}{16} \text{ A}.$$

$$V = 2(I_1 - I_2) = 2 \left(\frac{28}{16} + \frac{12}{16} \right) = 5 \text{ V}.$$

Problem 2.35 Simplify the circuit to the right of terminals (a, b) in Fig. P2.35 to find R_{eq} , and then determine the amount of power supplied by the voltage source. All resistances are in ohms.

Solution:


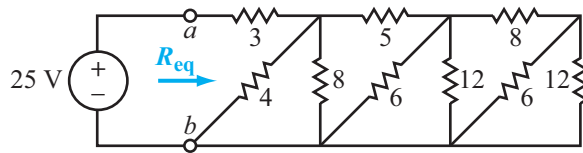
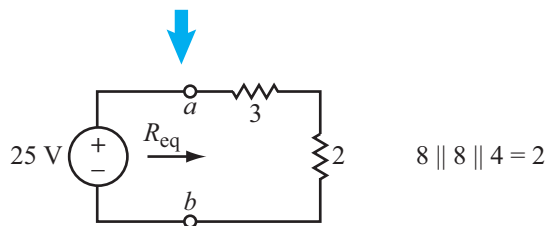
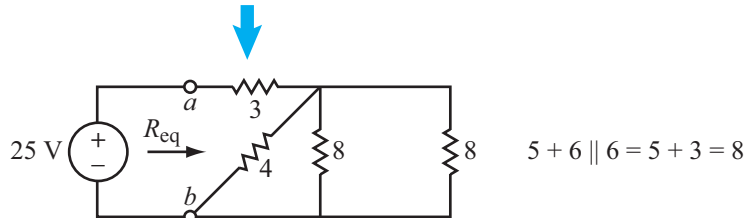
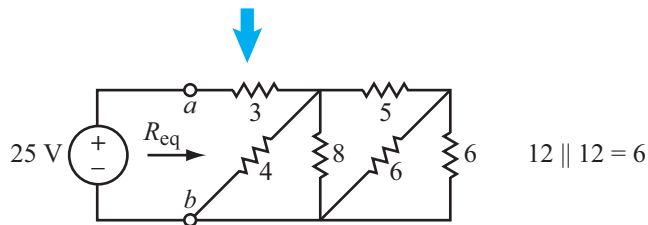


Figure P2.35: Circuit for Problem 2.35.

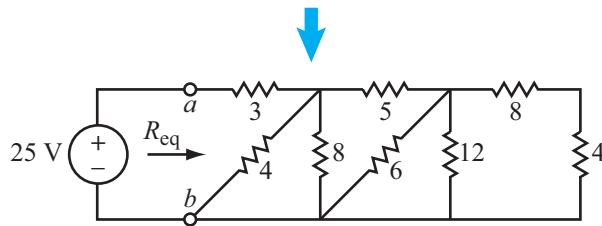


$$R_{eq} = 3 + 2 = 5 \, \Omega$$

$$P = \frac{V^2}{R_{eq}} = \frac{(25)^2}{5} = 125 \, \text{W}.$$

Problem 2.41 Find the power supplied by the generator in Fig. P2.41.

Solution:

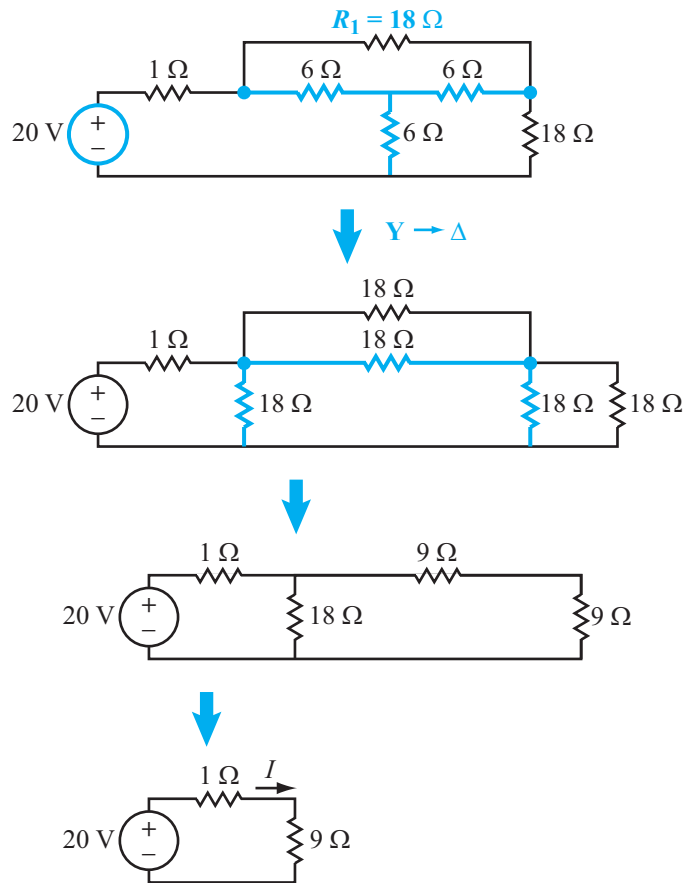


$$I = \frac{20}{10} = 2 \text{ A}$$

$$P = VI = 20 \times 2 = 40 \text{ W.}$$


Problem 2.43 Find I in the circuit of Fig. P2.43.

Solution:

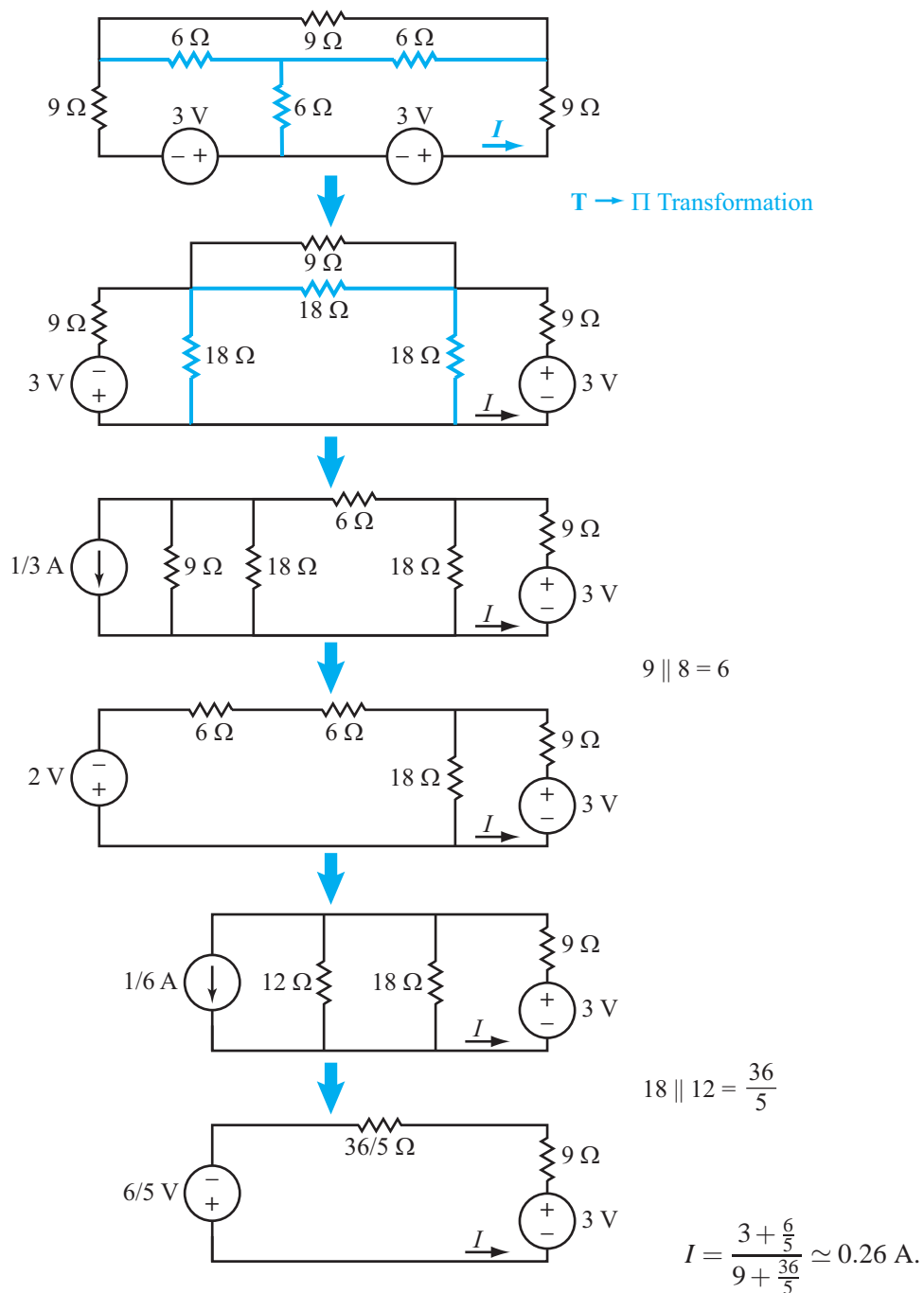


Problem 2.47 Find R_{eq} for the circuit in Fig. P2.47.

Solution:

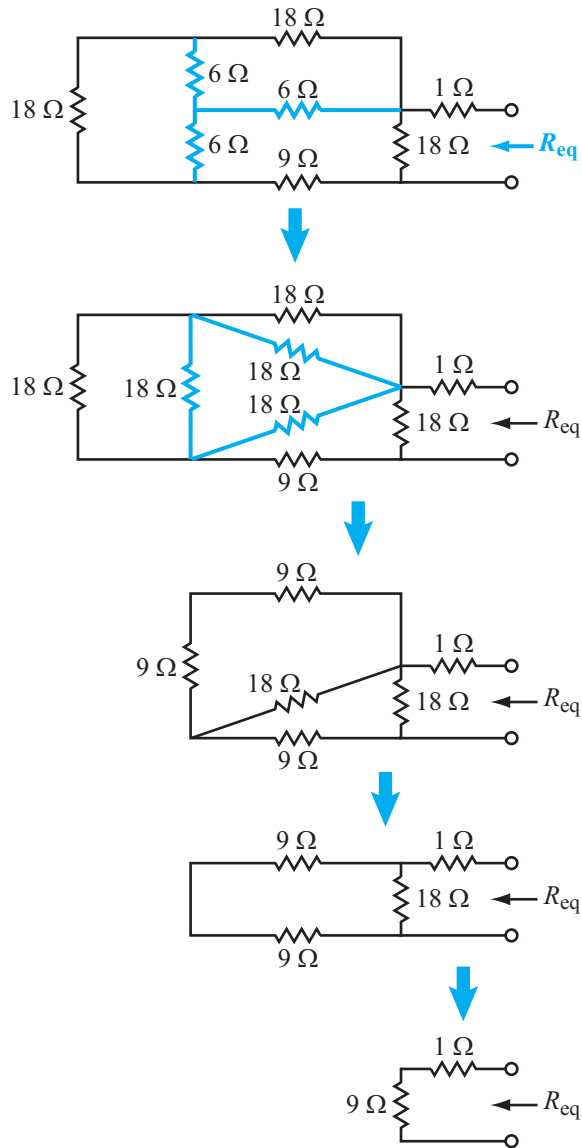

$$R_{eq} = 9 + 1 = 10\ \Omega.$$

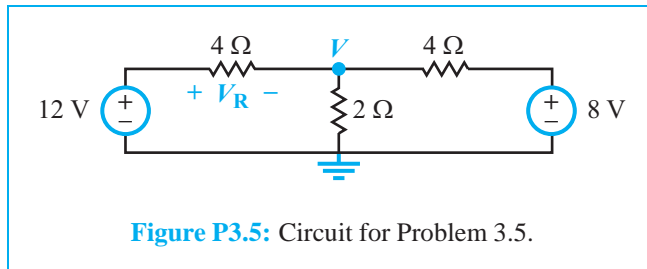Problem 3.5 Apply nodal analysis to determine the voltage V_R in the circuit of Fig. P3.5.



Solution: At node V :

$$\frac{V - 12}{4} + \frac{V}{2} + \frac{V - 8}{4} = 0,$$

which leads to

$$V = 5 \text{ V}.$$

Hence,

$$V_R = 12 - V = 12 - 5 = 7 \text{ V}.$$

Problem 2.52 Determine V_1 in the circuit of Fig. P2.52. Assume $V_F = 0.7$ V for all diodes.


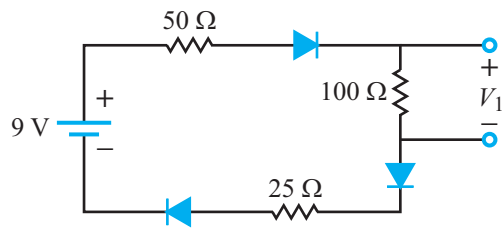


Figure P2.52: Circuit for Problem 2.52.

Solution:

$$I = \frac{9 - 3(0.7)}{50 + 100 + 25} \simeq 0.04 \text{ A},$$
$$V_1 = 100I = 4 \text{ V}.$$

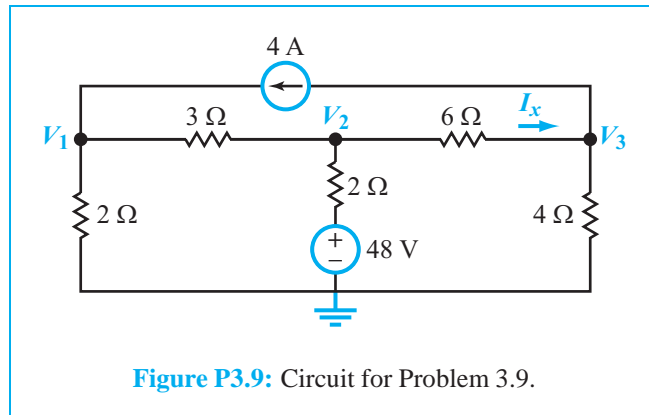Problem 3.9 Apply nodal analysis to find node voltages V_1 to V_3 in the circuit of Fig. P3.9 and then determine I_x .



Solution: At nodes V_1 , V_2 , and V_3 :

$$\text{Node 1: } \frac{V_1}{2} + \frac{V_1 - V_2}{3} - 4 = 0 \quad (1)$$

$$\text{Node 2: } \frac{V_2 - V_1}{3} + \frac{V_2 - 48}{2} + \frac{V_2 - V_3}{6} = 0 \quad (2)$$

$$\text{Node 3: } \frac{V_3 - V_2}{6} + \frac{V_3}{4} + 4 = 0 \quad (3)$$

Simplification of the three equations leads to:

$$5V_1 - 2V_2 = 24 \quad (4)$$

$$-2V_1 + 6V_2 - V_3 = 144 \quad (5)$$

$$-2V_2 + 5V_3 = -48 \quad (6)$$

Simultaneous solution of Eqs. (4)–(6) leads to:

$$V_1 = \frac{84}{5} \text{ V}, \quad V_2 = 30 \text{ V}, \quad V_3 = \frac{12}{5} \text{ V}.$$

Hence,

$$I_x = \frac{V_2 - V_3}{6} = \frac{30 - 12/5}{6} = 4.6 \text{ A}.$$