
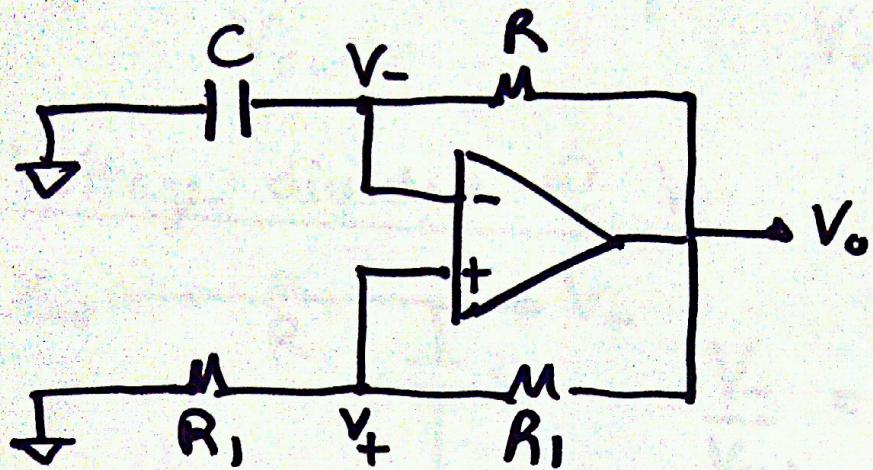


## Relaxation Oscillator Demystified

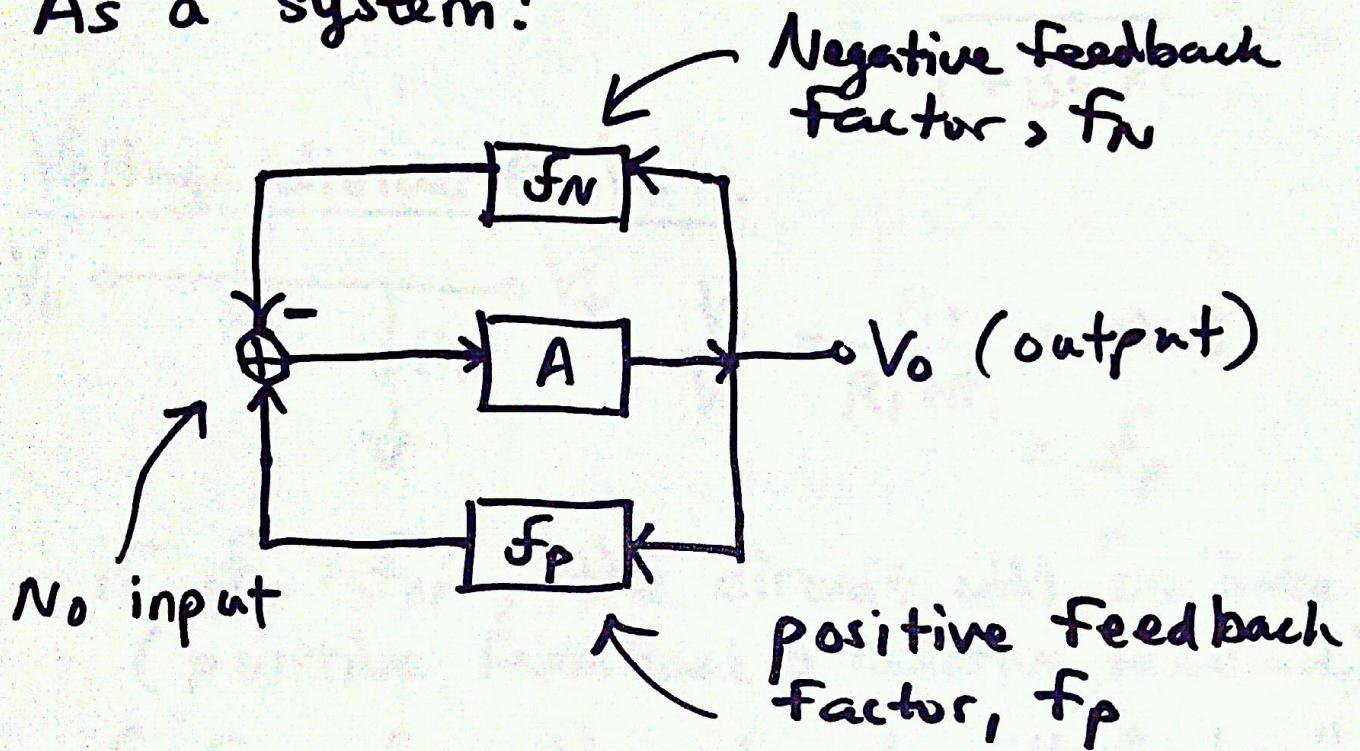


As a system:




$$f_N \triangleq \frac{V_-}{V_{out}}, \quad f_P \triangleq \frac{V_+}{V_{out}}$$

Voltage divider @ V<sub>-</sub>:

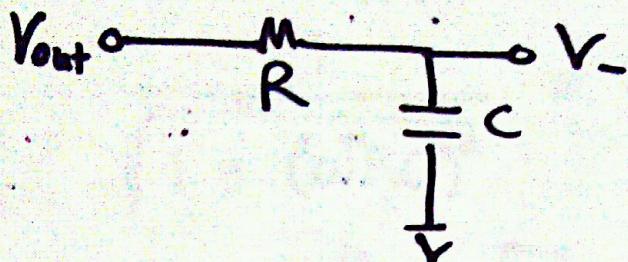

$$\begin{aligned} \frac{V_-}{V_{out}} &= \frac{1/j\omega C}{1/j\omega C + R} \\ &= \frac{1}{1 + j\omega RC} = f_N \end{aligned}$$

Voltage divider @ V<sub>+</sub>:

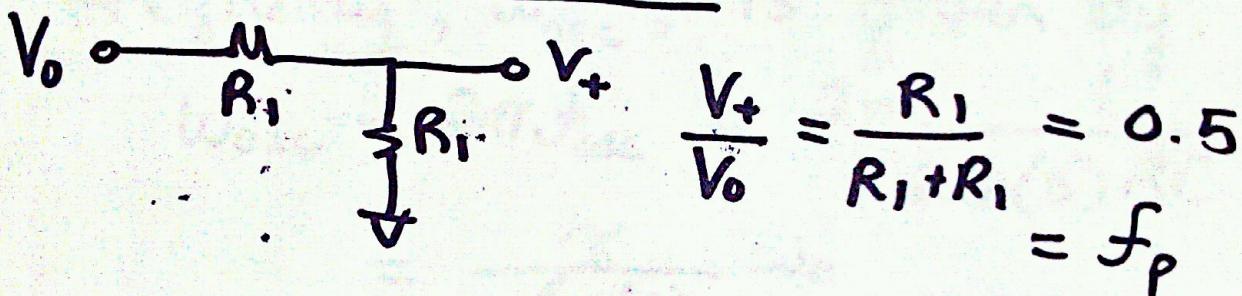

$$\begin{aligned} \frac{V_+}{V_0} &= \frac{R_1}{R_1 + R_2} = 0.5 \\ &= f_P \end{aligned}$$

if  $f_P > f_N$ , the circuit will "oscillate"  
(positive feedback > negative feedback)

if  $f_N > f_P$ , the circuit will "relax"  
(negative feedback > positive feedback)

At some frequency,  $\omega^*$ , the circuit transitions from (-) FB to (+) FB.

$$|f_N| = |f_P|$$

$$\frac{1}{\sqrt{1 + (\omega^* RC)^2}} = 0.5$$

$$\omega^* = \frac{\sqrt{3}}{RC} = \sqrt{3} \cdot \omega_0 ; \omega_0 = \frac{1}{RC}$$

We are told that the oscillation frequency,  $\omega_{osc}$ , is given by:

$$\omega_{osc} = 2\pi f_{osc} = 2\pi \cdot \frac{1}{2\ln(3)RC}$$

$$= \frac{\pi}{\ln(3)} \omega_0$$

Since the circuit oscillates, we expect that  $\omega_{osc} > \omega^*$

$$\omega_{osc} = \frac{\pi}{\ln(3)} \omega_0 \approx 2.86 \omega_0$$

$$\omega^* = \sqrt{3} \omega_0 \approx 1.73 \omega_0$$

~~Ques~~ So  $\omega_{osc} > \omega^*$  as expected ✓

IF we assume that  $\frac{V_{CC}}{|A|} \approx 0$

(which is not a bad assumption)  
since  $A \approx 10^6$  and  $V_{CC} \approx 10V$

then

$$V_{out} = \begin{cases} +V_{CC} & (V_+ - V_-) > 0 \\ -V_{CC} & (V_+ - V_-) < 0 \end{cases}$$

When  $V_{out} = +V_{CC}$

- C charges from its initial voltage to  $(V_{CC} - V_{initial})$  as long as  $V_{out} = +V_{CC}$
- $V_+ = 0.5 V_{out} = 0.5 V_{CC}$


When  $V_{out} = -V_{CC}$

- C discharges from  $V_{initial}$  towards  $-V_{CC}$  as long as  $V_+ - V_- < 0$
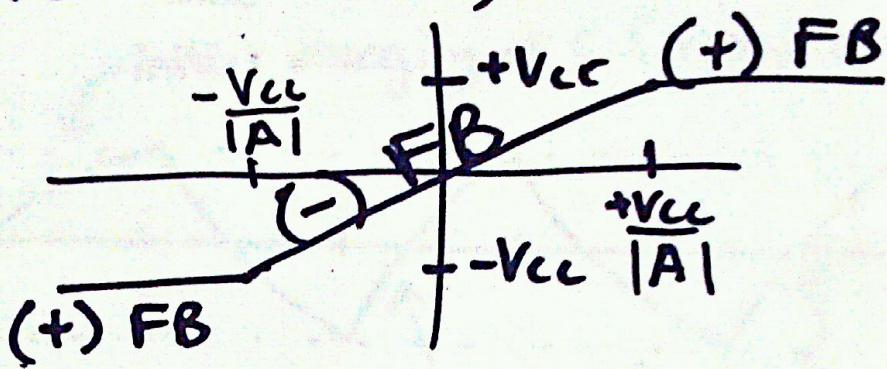
## Sketching the output


Since the circuit oscillates  
(i.e. it is in positive FB)

$V_{out}$  can only take on  $+V_{cc}$  or  
 $-V_{cc}$  (assuming an ideal op amp  
transfer curve)



$$V_{out} = \begin{cases} +V_{cc} & |A|(V_+ - V_-) > +V_{cc} \\ -V_{cc} & |A|(V_+ - V_-) < -V_{cc} \end{cases}$$

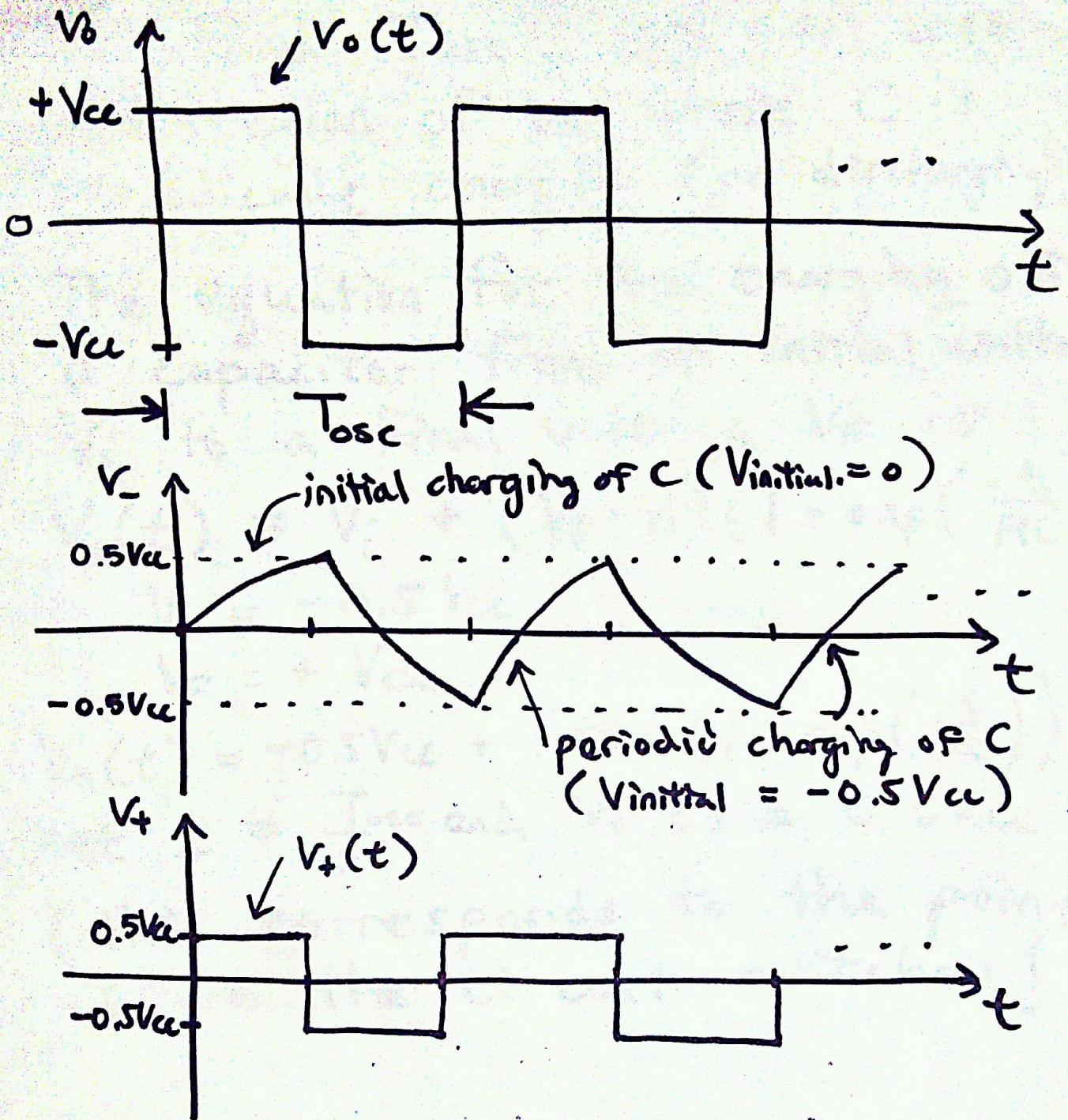The switching frequency  
(oscillation frequency) will be  
determined by  $V_+ - V_-$



To find  $T_{osc}$ , we can use the region of  $V_c$  where  $C$  is periodically charging (or discharging)

The equation for the charging of a capacitor from an initial voltage  $V_i$  to a final voltage  $V_f$  is:

$$V_o(t) = V_i + (V_f - V_i) \left( 1 - \exp\left(\frac{-t}{RC}\right) \right)$$

$$V_i = -0.5V_{cc}$$

$$V_f = +V_{cc}$$

$$V_o(t) = -0.5V_{cc} + 1.5V_{cc} \left( 1 - \exp\left(\frac{-t}{RC}\right) \right)$$

$$\text{set } t = \frac{T_{osc}}{2} \text{ and } V_o(t) = 0.5V_{cc}$$

(this corresponds to the point where the circuit switches!)

$$0.5\hat{V_{CC}} = -0.5\hat{V_{CC}} + 1.5\hat{V_{CC}} \left(1 - \exp\left(-\frac{T_{osc}}{2RC}\right)\right)$$

$$1 = 1.5 \left[-\exp\left(-\frac{T_{osc}}{2RC}\right) + 1\right]$$

$$\begin{aligned} 2 &= 3 \left[1 - \exp\left(-\frac{T_{osc}}{2RC}\right)\right] \\ &= 3 - 3 \exp\left(-\frac{T_{osc}}{2RC}\right) \end{aligned}$$

$$3 \exp\left(-\frac{T_{osc}}{2RC}\right) = 1$$

$$\exp\left(-\frac{T_{osc}}{2RC}\right) = \frac{1}{3}$$

$$\ln \left[ \frac{1}{3} \right] = \ln \left[ \frac{1}{e^{\frac{T_{osc}}{2RC}}} \right]$$

$$-\frac{T_{osc}}{2RC} = \ln\left(\frac{1}{3}\right) = -\ln(3)$$

$$T_{osc} = 2\ln(3)RC$$

$$\text{so } f_{osc} = \frac{1}{T_{osc}} = \frac{1}{2\ln(3)RC}$$