

Final Review Problem #1: Common Collector Amplifier (BJT)

otherwise known as "Emitter follower" or "voltage follower"


The main objective of this problem is to prove the advantage of using a voltage follower (buffer) in a circuit.

Mainly, a voltage follower has a gain of ≈ 1 , which means $\Delta V_{out} \approx \Delta V_{in}$.


A gain of ≈ 1 seems pretty boring. However, it has a very high input impedance and a very low output impedance, which will help us a lot with impedance matching.

(e.g. You can drive an $8\text{-}\Omega$ speaker or a motor with these things if you are careful enough.)

So here is the topology:

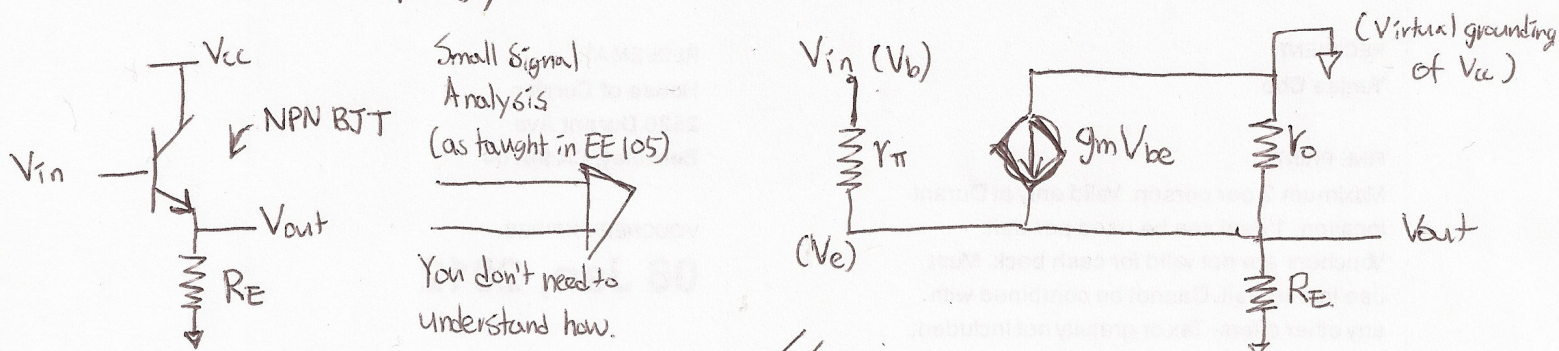

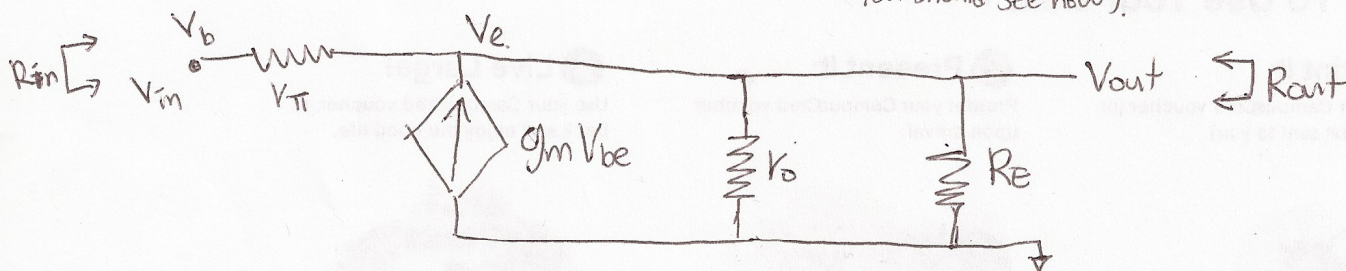One more Simplification
(You should see how).



Easier: ① Write an expression for $gain = \frac{V_{out}}{V_{in}}$

Then use these values to approximate the gain: (chosen to make the math easier)

$$g_m = \frac{I_c}{V_T} \quad r_o = \frac{V_A}{I_c} \quad r_{\pi} = \frac{\beta}{g_m} \quad I_c = 1 \text{ mA} \quad V_T \approx 25 \text{ mV} \quad V_A = 100 \text{ V} \quad \beta = 100, R_E = 10 \text{ k}\Omega$$

Is your gain ≈ 1 ?

from here, you can assume: $\frac{1}{g_m} \ll r_o$

Harder: ② Calculate R_{in} . (You can't ground V_{out} !)

(hint: apply a test source at V_{in} and relate V_b and V_e)

Sanity check: Is your R_{in} big? (greater than $1 \text{ k}\Omega$).

③ Calculate R_{out} :

(hint: Short V_{in} to GND and apply a test source at V_{out}).

Sanity check: Is your R_{out} small? (smaller than $1 \text{ k}\Omega$)

If you can solve these problems, you are in an awesome shape for EE105.