

“I believe in intuitions and inspirations...I sometimes FEEL that I am right. I do not KNOW that I am.”

— Albert Einstein

Filter Intuitions

April 6th, 2012

Yunjae Cho

Photo credits to:

Neel Shah (Summer 2011)

Michel Maharbiz (Fall 2011)

Vivek Subramanian

Circuit Intuition

Circuit? Intuitive? What??? lol

Believe it or not, circuits can be *intuitive*

These exercises are designed to build your **qualitative intuition** in identifying different types of filters.

Impedance, $Z(w)$ is a function of w :

$$Z_R(w) = R, Z_C(w) = 1/jwC, Z_L(w) = jwL$$

Low (~DC) frequency:

$$Z_C(0) = \text{infinity}$$

$$Z_L(0) = 0$$

High (~infinity) frequency:

$$Z_C(\text{inf}) = 0$$

$$Z_L(\text{inf}) = \text{infinity}$$

Try not to write down any equations during this exercise.

Rather, examine the filter outputs for inputs with:

Low frequencies (0 Hz)

Middle frequencies

High frequencies (inf)


In case you're a visual person like me, :)

	Low Frequency (e.g. $w=0$)	High Frequency (e.g. $w=1$ GHz)
Capacitor	Block!	Pass!
Inductor	Pass!	Block!

Your good intuition might save you some time on exam / circuit designs


Circuit Intuition (RC)

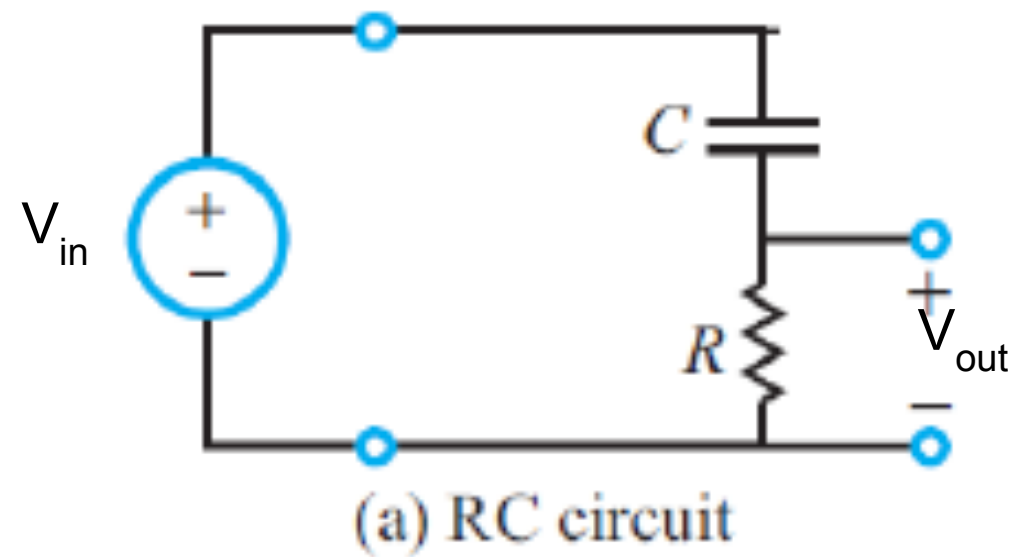Let's warm up with a simple one mokay... what about this one?




Is this:

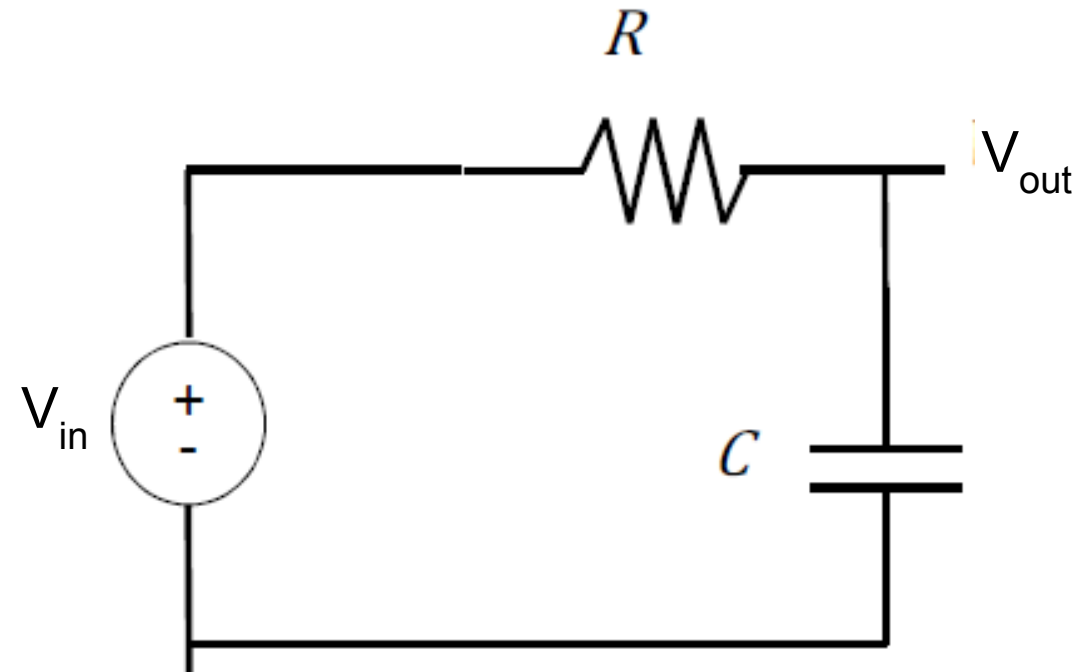1. High-Pass Filter
2. Low-Pass Filter
3. Band-Pass Filter
4. Band-Reject Filter
5. I-don't-know Filter



1. High-Pass Filter
2. Low-Pass Filter
3. Band-Pass Filter
4. Band-Reject Filter
5. I-don't-know Filter

Circuit Intuition (RC)

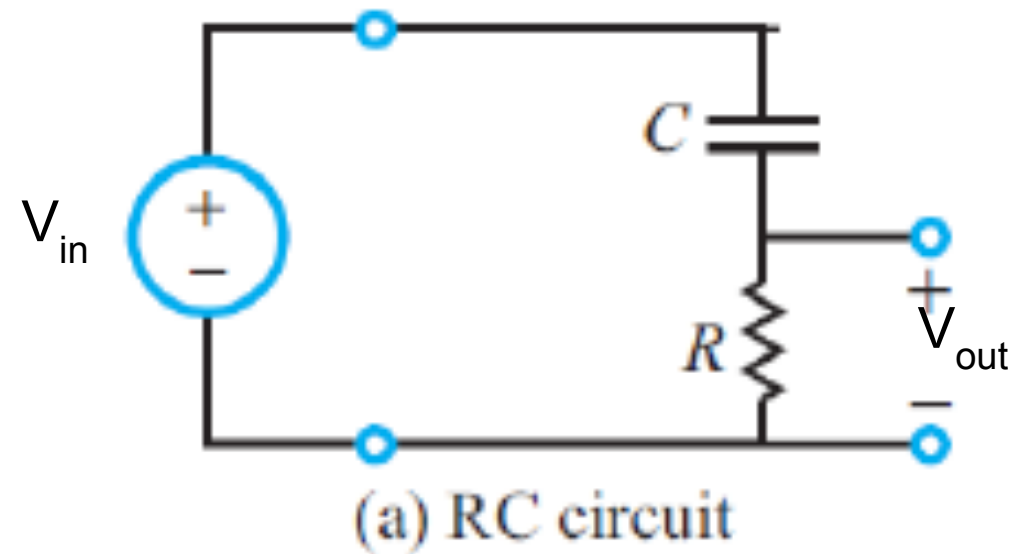

$V_{out} = V$ drop across R

Low-frequency Input:
reach V_{out} node?

High-frequency Input:
reach V_{out} node?

Still not convinced?
Draw equivalent circuits for
both cases

answer: HP

	Low Frequency (e.g. $\omega=0$)	High Frequency (e.g. $\omega=1$ GHz)
Capacitor	Block!	Pass!
Inductor	Pass!	Block!

Circuit Intuition (RC)

Similar logic applies here:

High-frequency Input:

Cap = short-circuit (wire)

$V_{out} = \text{GND}$

V_{in} is "shorted" to GND


Low-frequency Input:

Cap = open-circuit

=> No current through R

=> $V_{out} = V_{in}$


Answer: LP

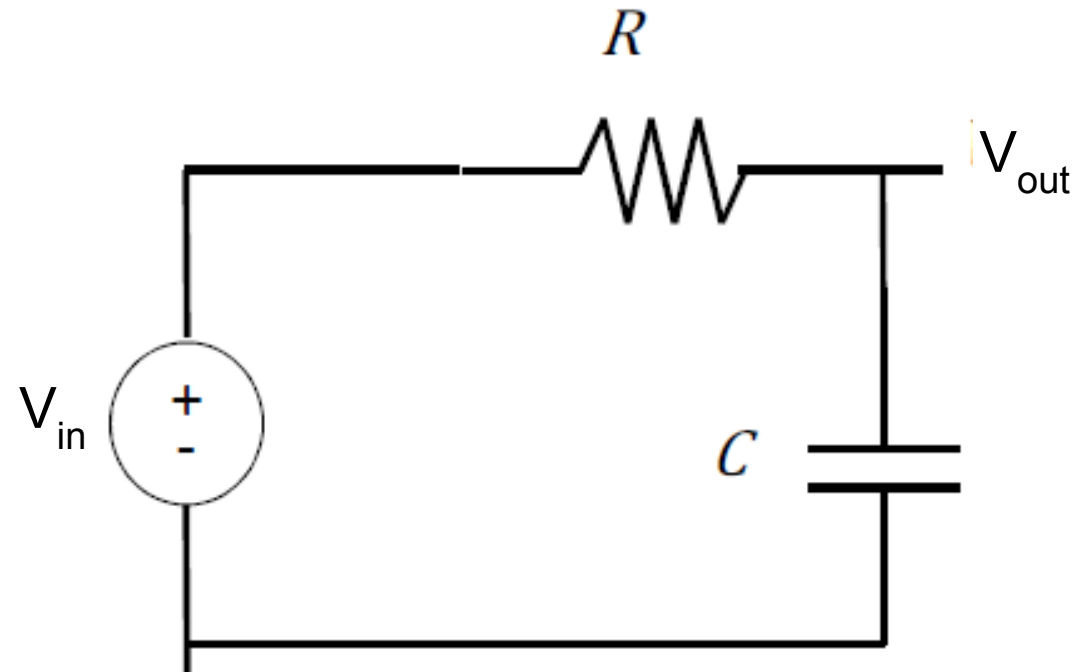


	Low Frequency (e.g. $\omega=0$)	High Frequency (e.g. $\omega=1$ GHz)
Capacitor	Block!	Pass!
Inductor	Pass!	Block!

Circuit Intuition (RL) (still 1st order)

What about inductors?

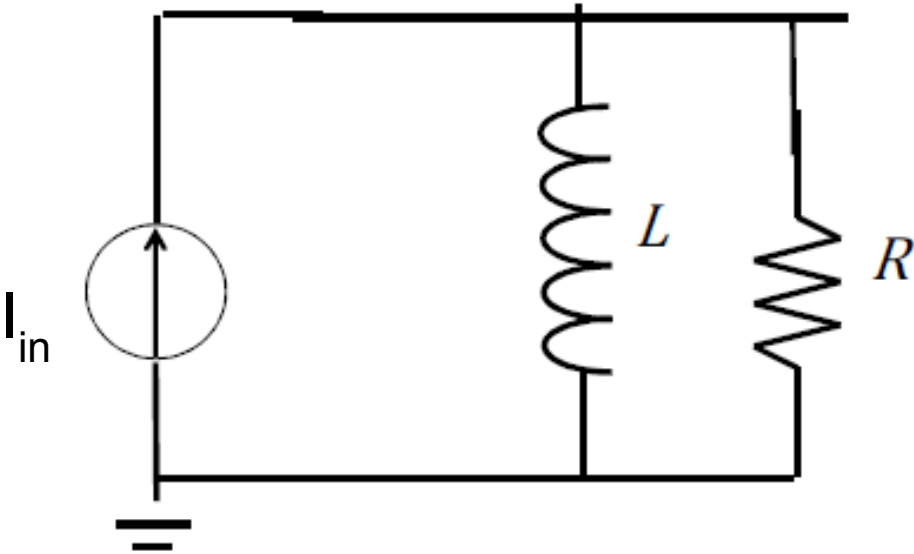

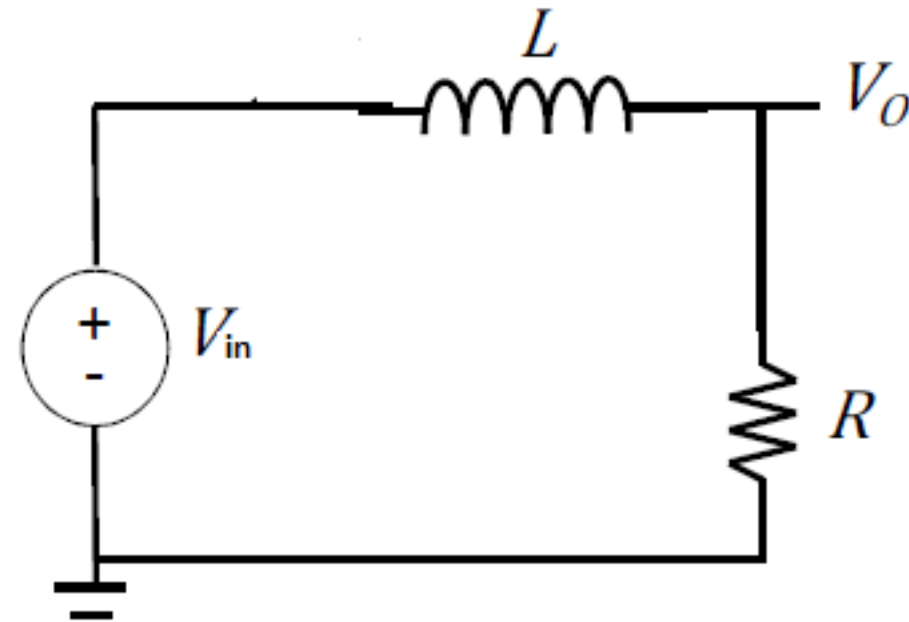
1. High-Pass Filter
2. Low-Pass Filter
3. Band-Pass Filter
4. Band-Reject Filter
5. I-don't-know Filter



	Low Frequency (e.g. $\omega=0$)	High Frequency (e.g. $\omega=1$ GHz)
Capacitor	Block!	Pass!
Inductor	Pass!	Block!

Circuit Intuition (RL) (still 1st order)


What about inductors?

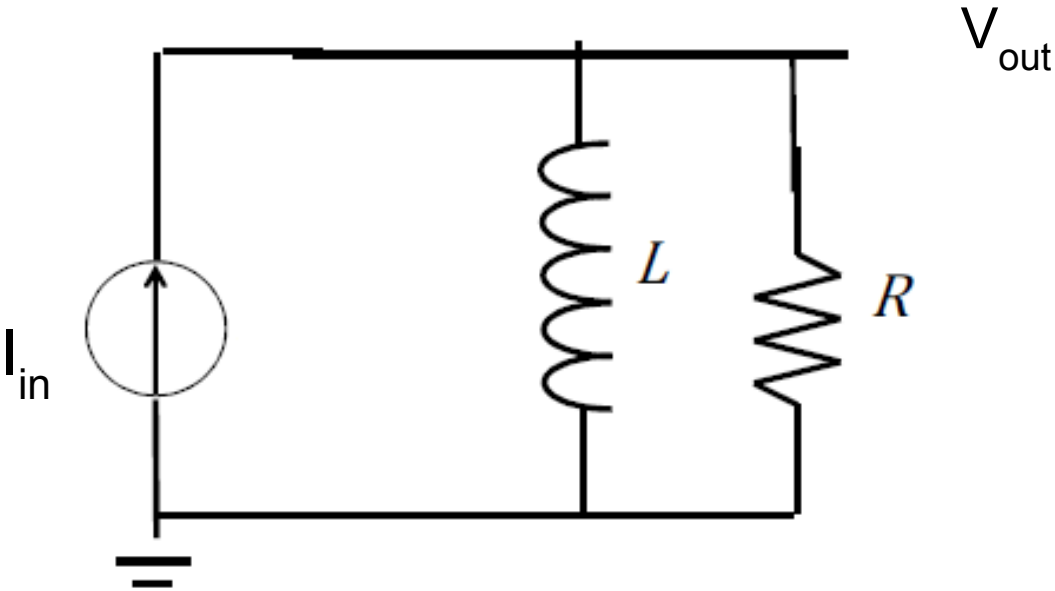

Low-frequency Input:
Inductor = short circuit (wire)

High-frequency Input:
Inductor = open-circuit

answer: HP

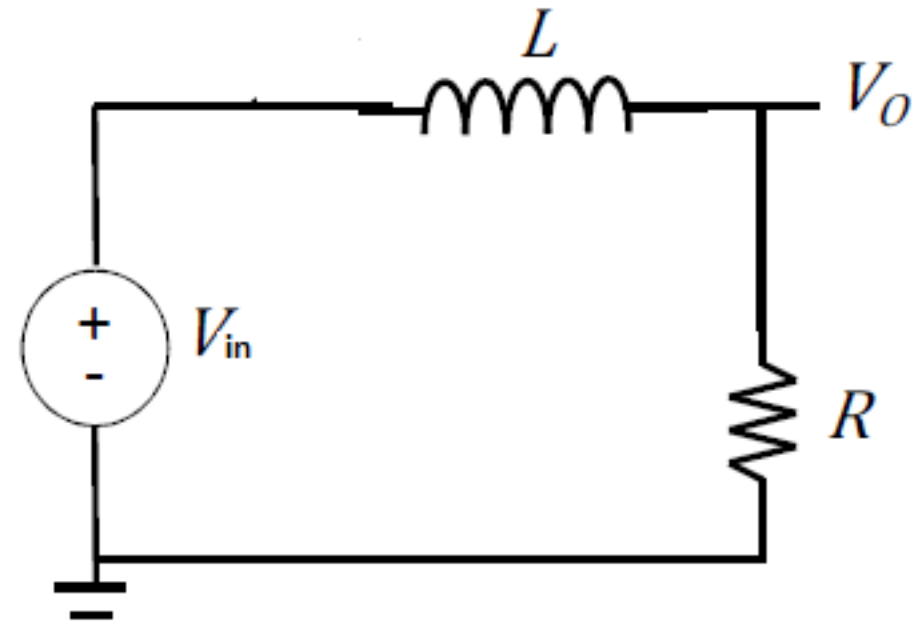

	Low Frequency (e.g. $\omega=0$)	High Frequency (e.g. $\omega=1$ GHz)
Capacitor	Block!	Pass!
Inductor	Pass!	Block!

answer: LP

Circuit Intuition (RLC - 2nd Order)


What kind of filter is this circuit?

A = Low pass filter

C = Band pass filter

B = High pass filter

D = Band stop filter

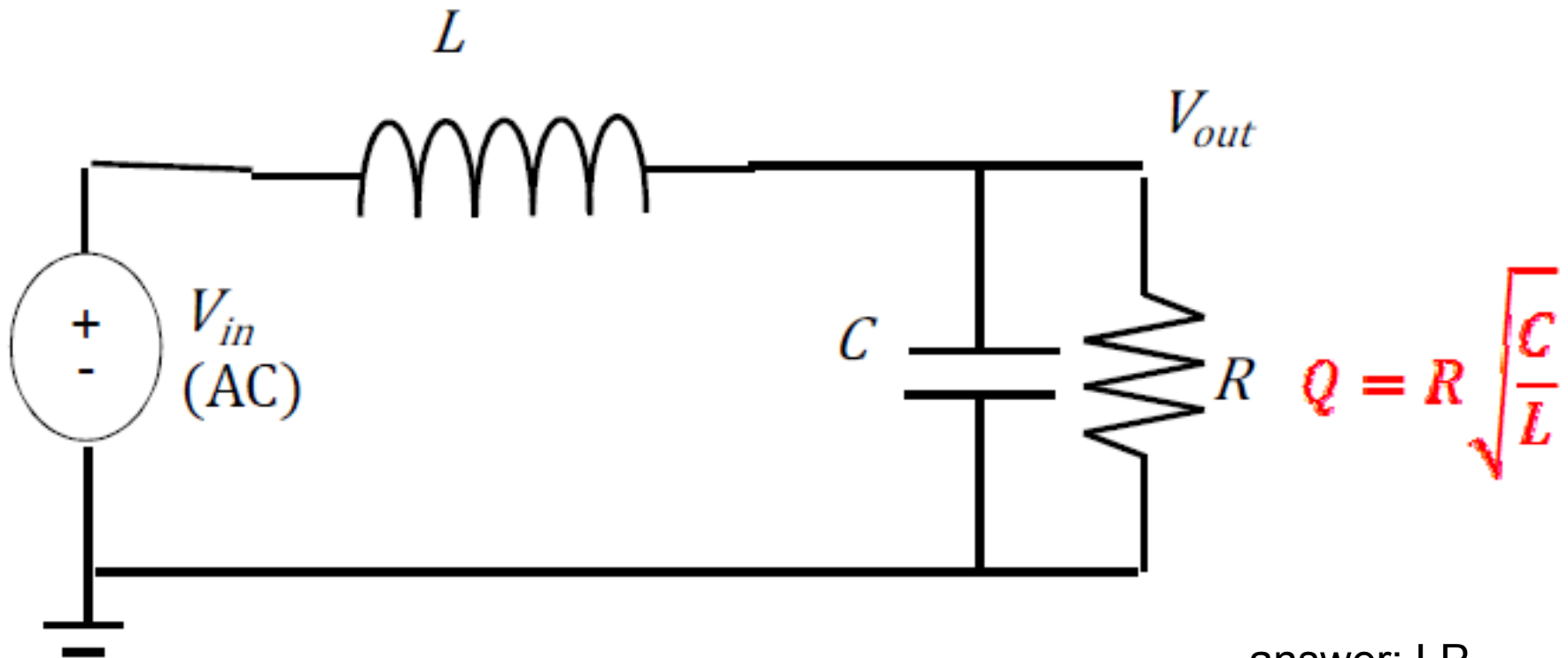

answer: LP

Circuit Intuition (RLC - 2nd Order)


What kind of filter is this circuit?

A = Low pass filter

C = Band pass filter

B = High pass filter



D = Band stop filter

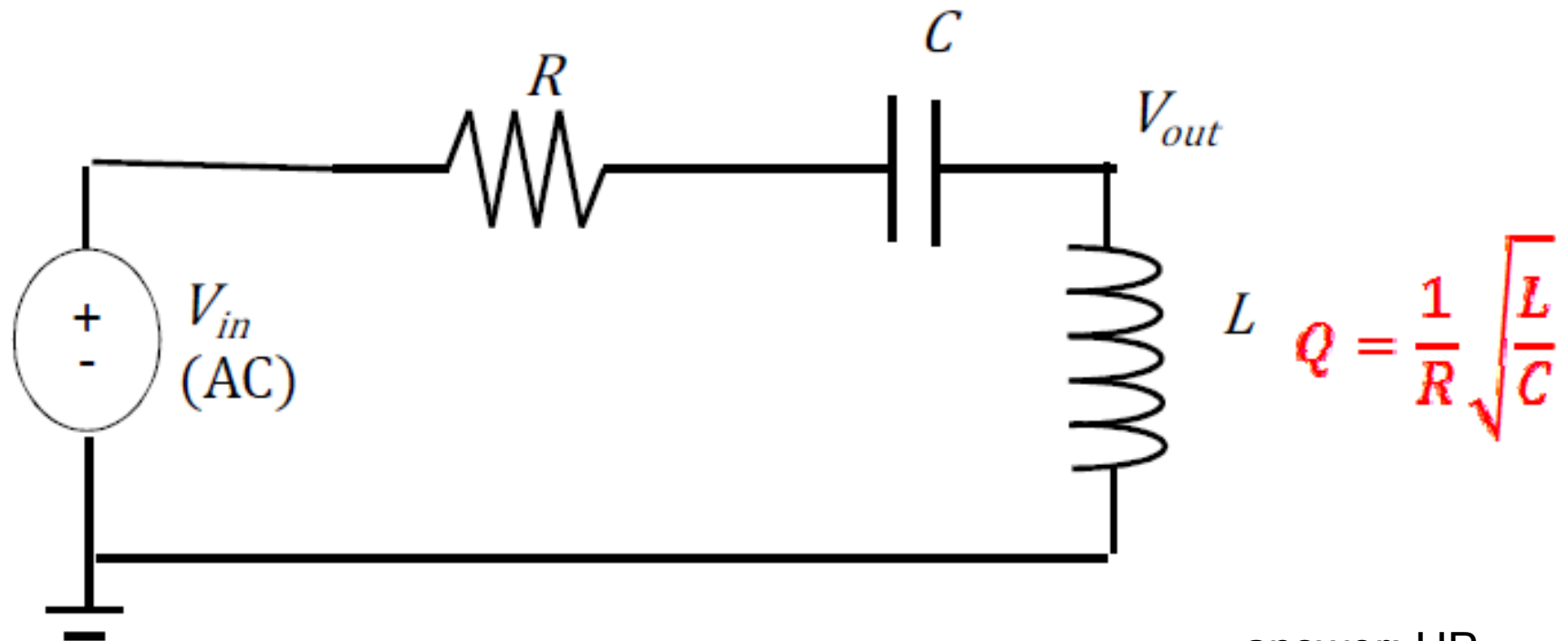

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

answer: HP

Circuit Intuition (RLC - 2nd Order)

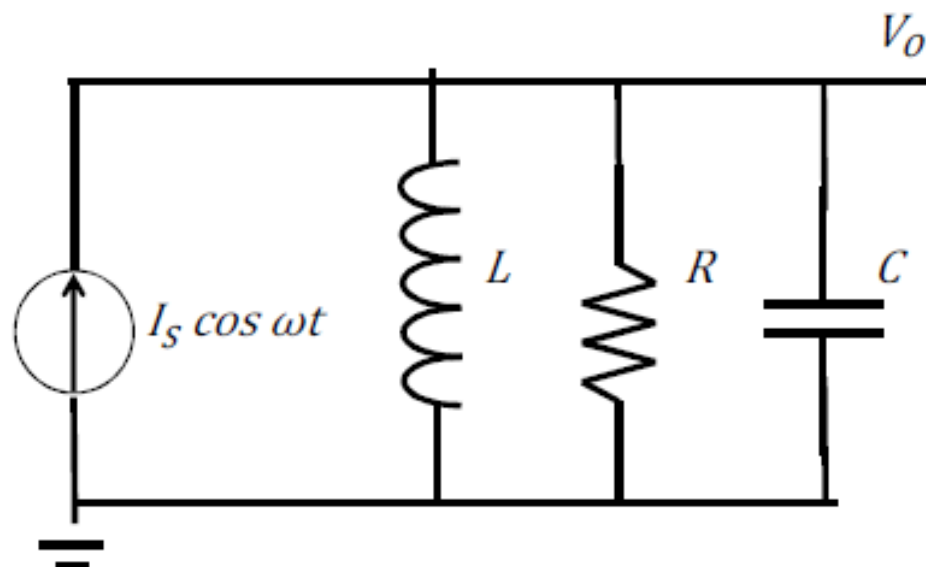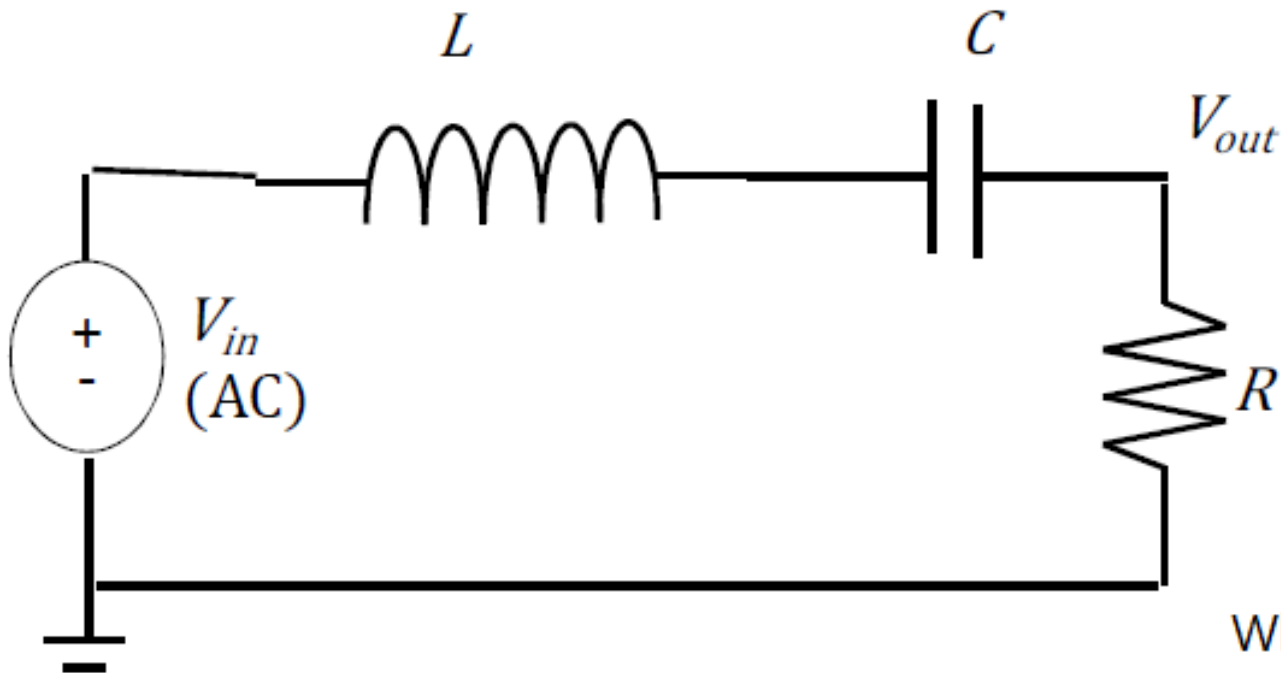

What Kind of Filter are they?

A = Low pass filter

B = High pass filter

C = Band pass filter

D = Band stop filter

Hint: They are the same type


answer: BP

Circuit Intuition (RLC - 2nd Order)

- What kind of filter is this circuit?


- A = Low pass filter
- B = High pass filter
- C = Band pass filter
- D = Band stop filter

Darn it, I just gave it away! lol

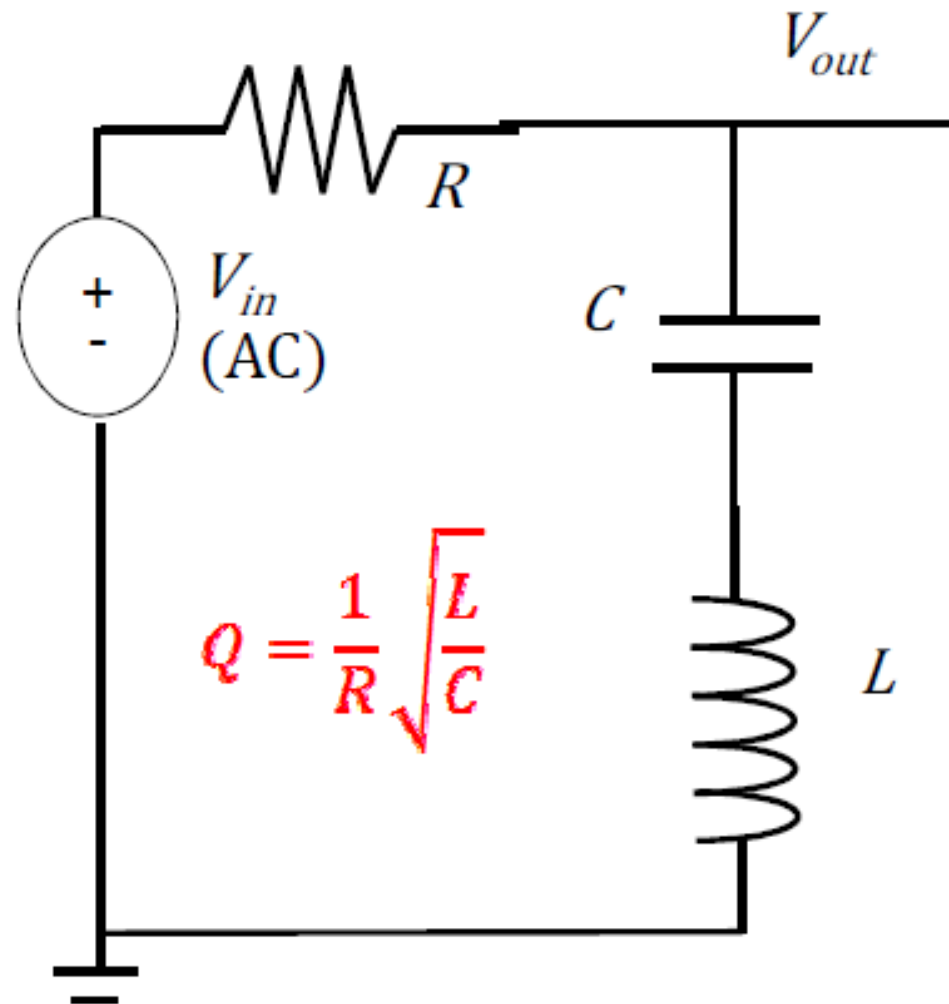

Circuit Intuition (RLC - 2nd Order)

Now you can tell me what this one is:

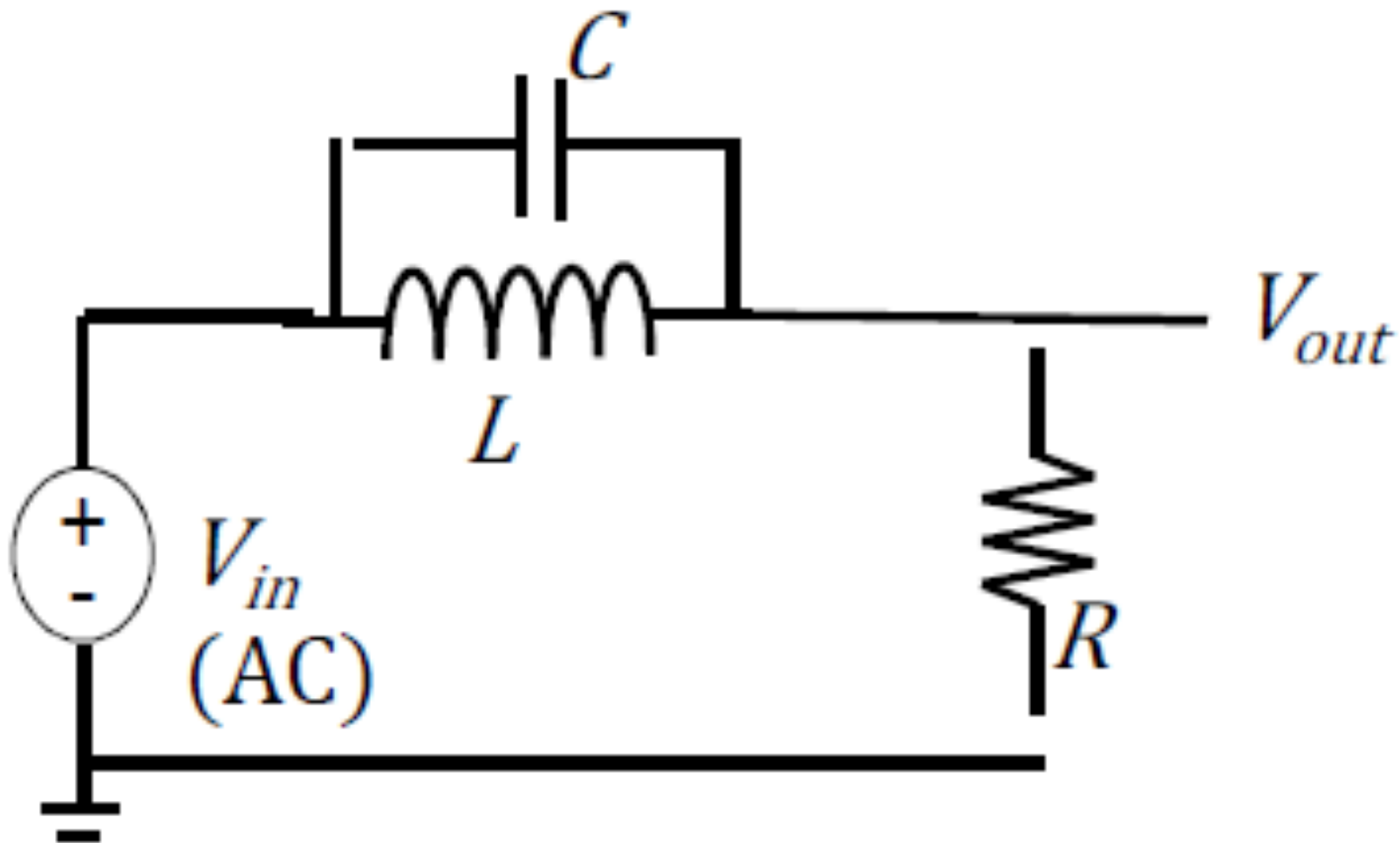


Guess what, this is the same type as the last one (Band-Reject)

Active Filtering

Filtering with Op Amps:

Advantage: can have a Gain! => Amplify Input Signal!

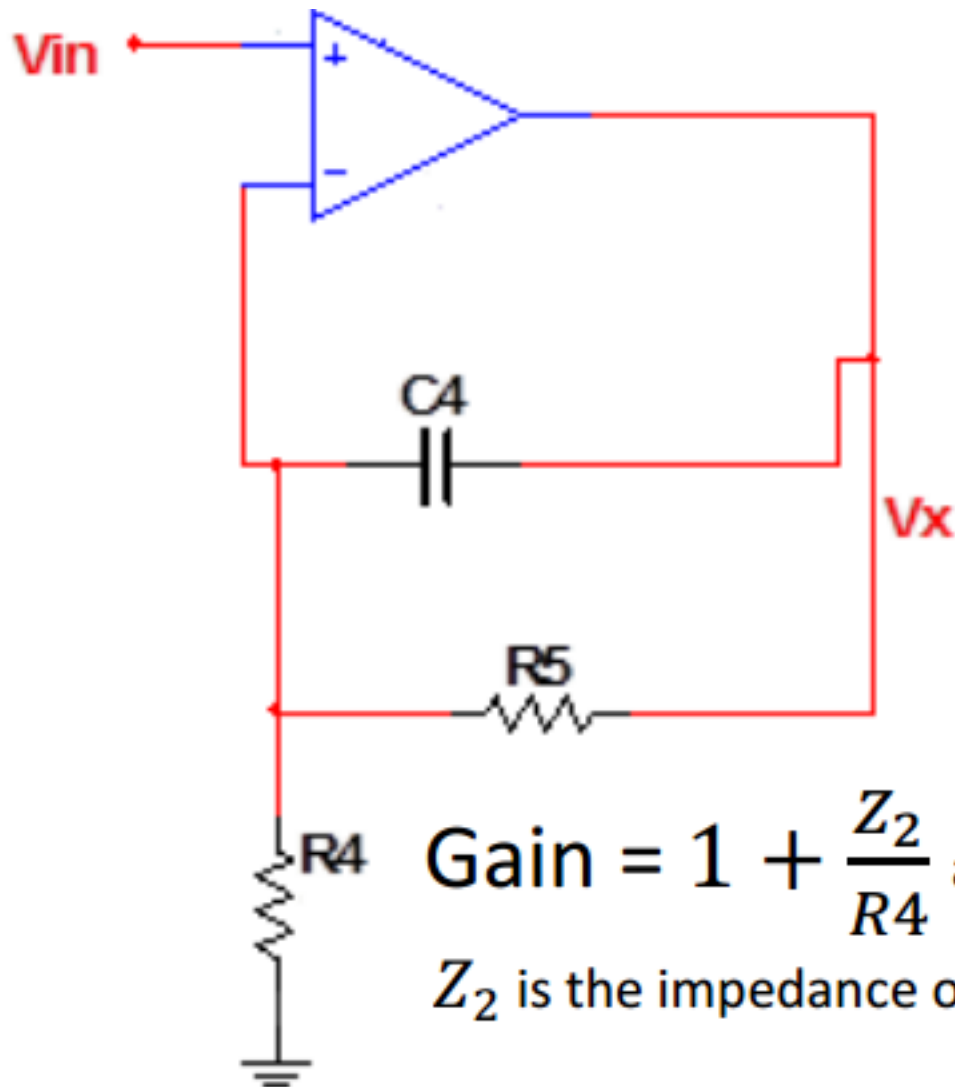From the Final Project - Non-inverting Low Pass Filter



$$\text{Gain} = 1 + \frac{Z_2}{R4} \text{ and } \omega_c = 1000 \text{ rad/sec and the DC gain is 100}$$


Z_2 is the impedance of $C4$ and $R5$ in parallel.

Active Filtering


From the project - Notch Filter

You've proven the two circuits are equivalent (gyrator)

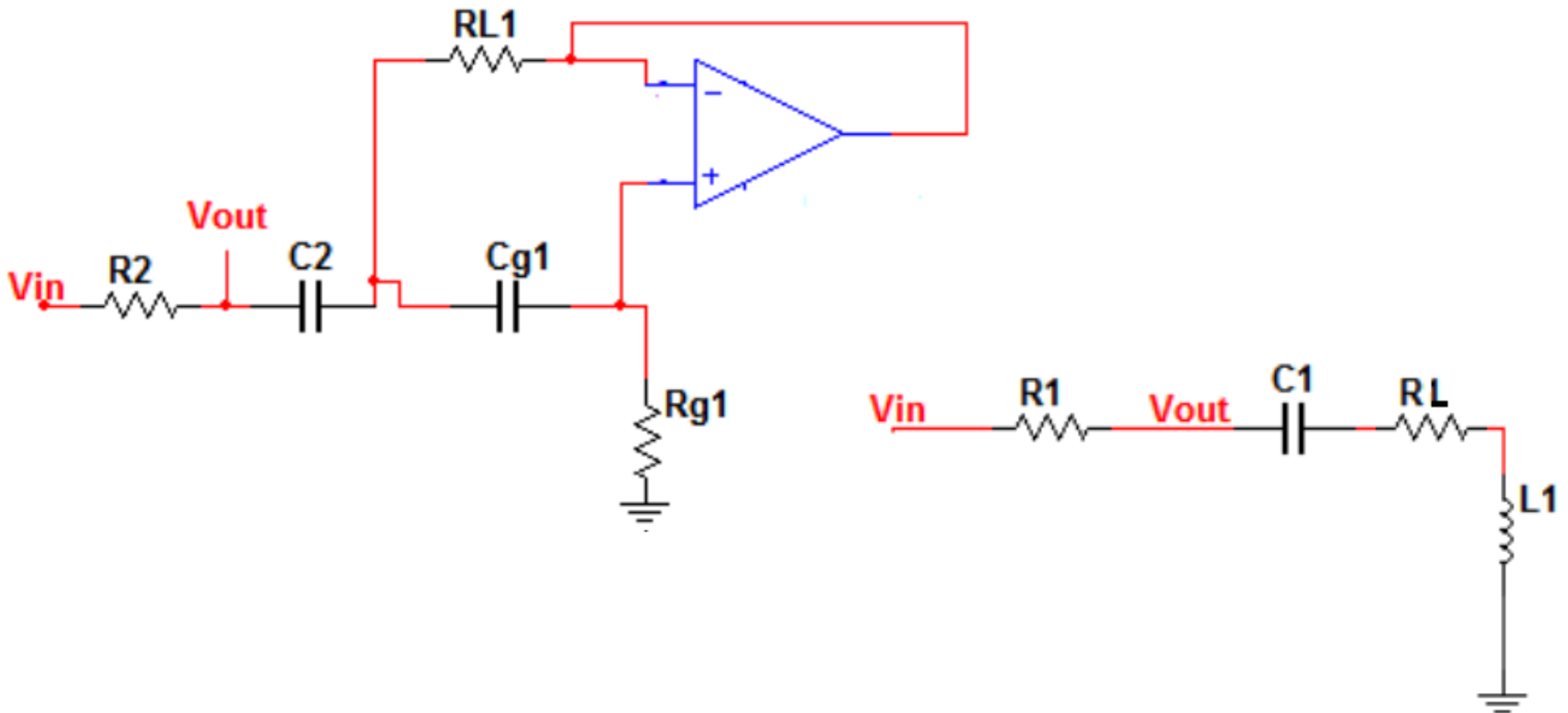Makes sense why it's a Notch Filter, now?




Active Filtering

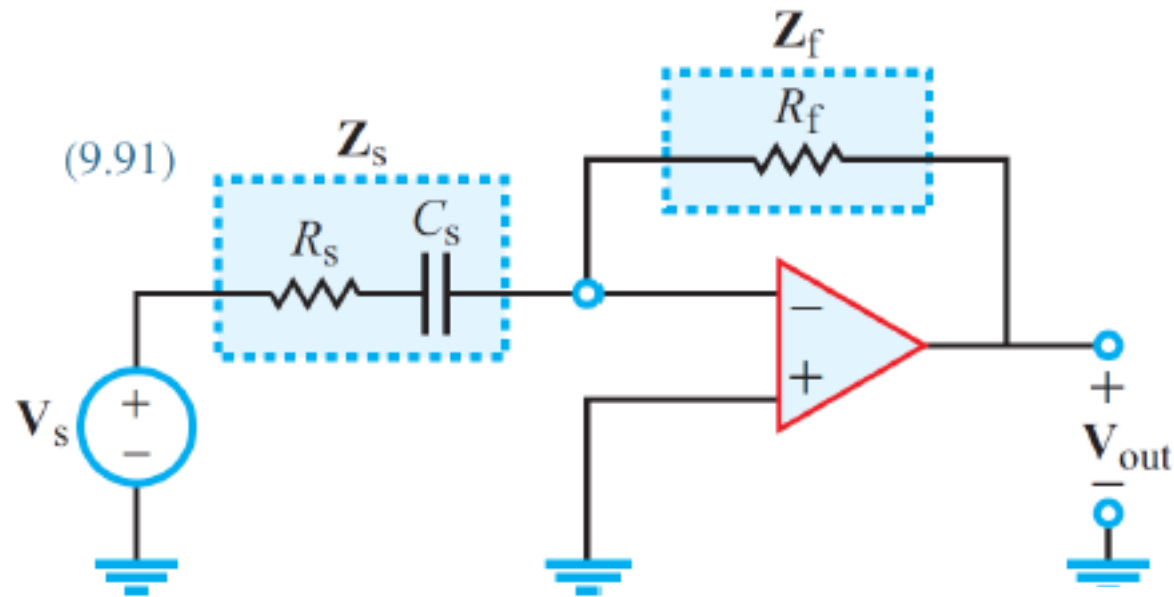

Inverting Differentiator


High Pass or Low Pass?

Inverting Integrator

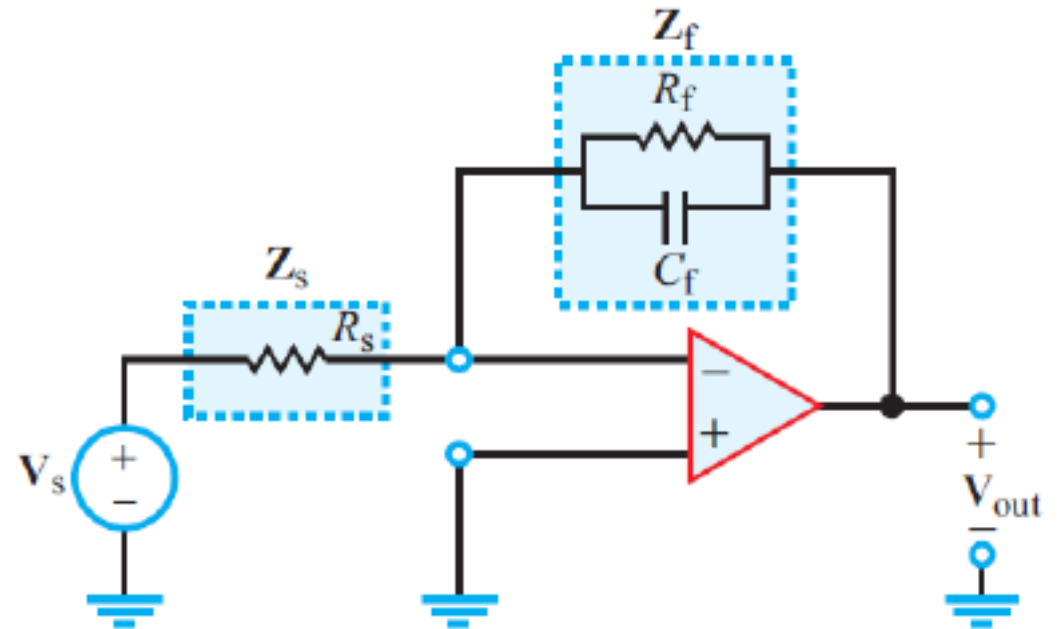

Active Filtering (Cascading)

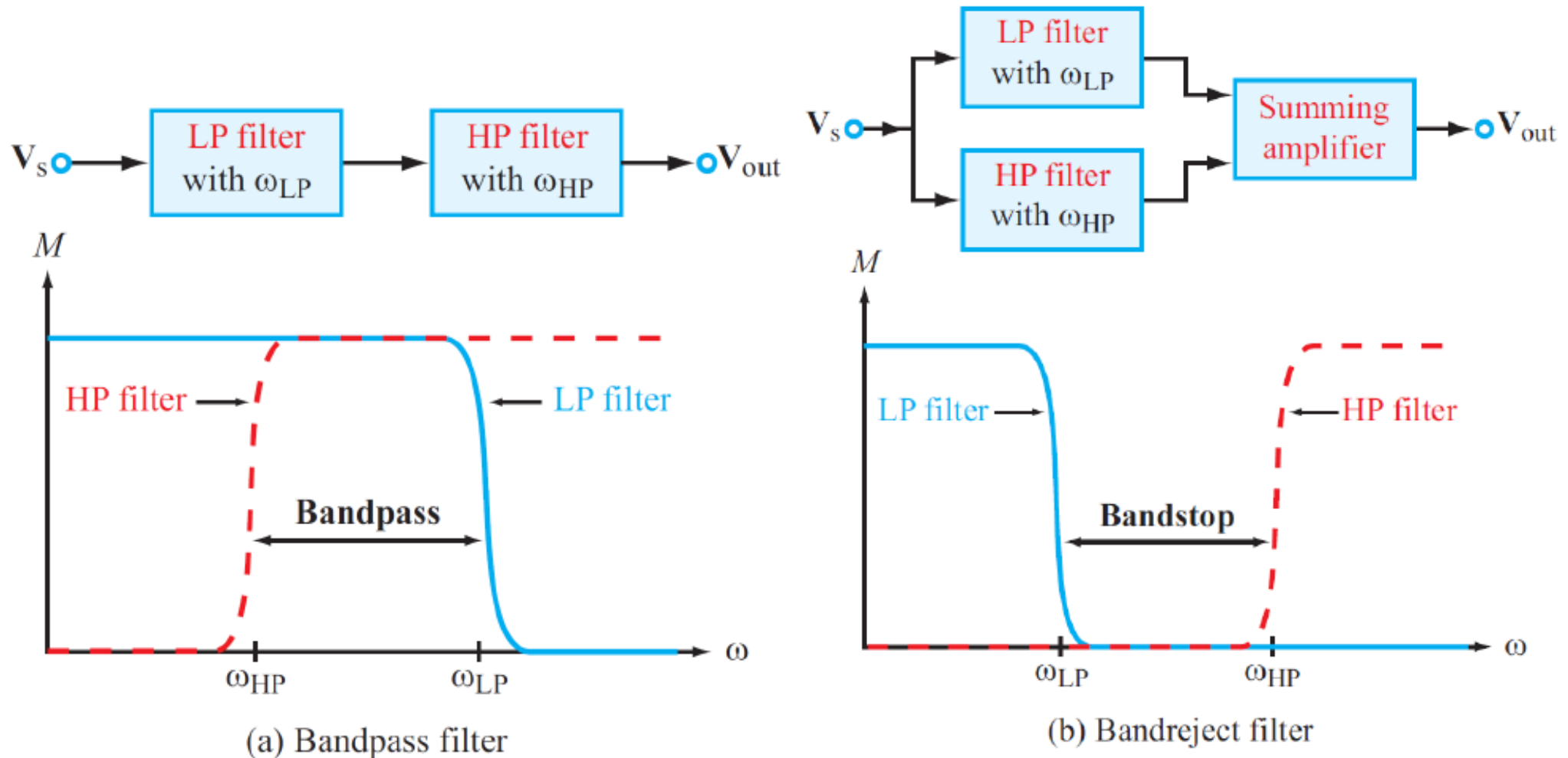
You can't do this by combining simple circuit elements in some kind of order without any Op Amps. (why?)



Filters combined in Series : Multiply transfer functions

Filters combined in Parallel : Add transfer functions

Cascaded Filters

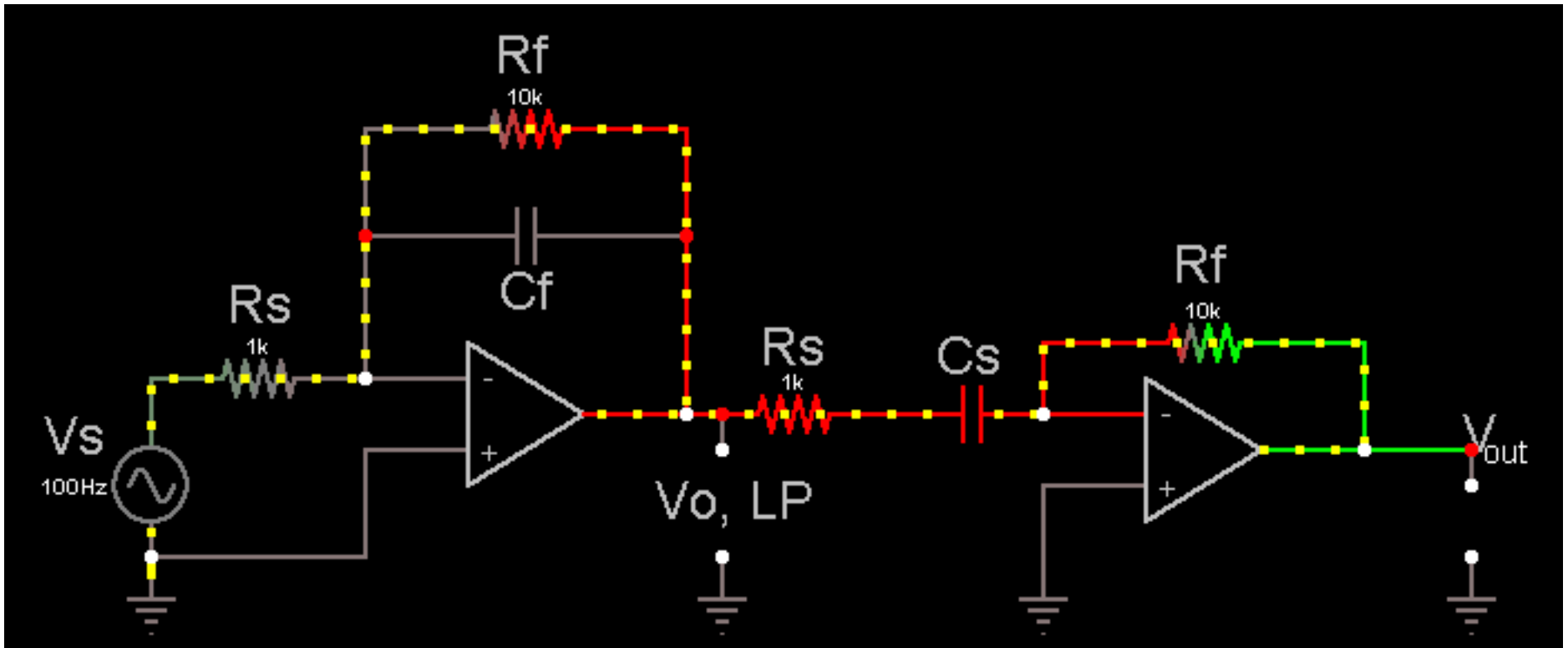

Determine the type of the gigantic filter above
(Determine the type of each sub-filter then
cascade them)

Possible Application:
Designing a hearing aid for human voice range
(50 Hz ~ 20 kHz)

Inverting Amplifier

