

HW 1

EE40

Maharbiz

Spring 2012

Posted Monday 1/30/2012


Due Monday 2/6/2012

1. A steady flow resulted in 3×10^{15} electrons entering a device in 0.1 ms. What is the current?
2. Determine the current $i(t)$ flowing through a certain device if the cumulative charge that has flowed through it up to time t is given by


- (a) $q(t) = 3.6t$ [mC]
- (b) $q(t) = 5\sin(377t)$ [mC]
- (c) $q(t) = 0.3[1 - e^{-0.4t}]$ [pC]
- (d) $q(t) = 0.2t \sin(120\pi t)$ [nC]

3. The plot below displays the cumulative amount of charge $q(t)$ that has entered a certain device up to time t . What is the current at

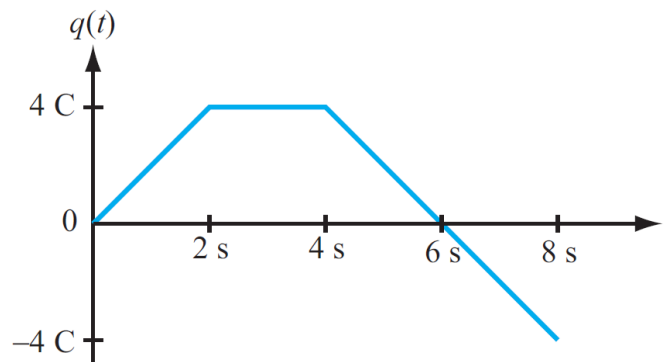- (a) $t = 1$ s
- (b) $t = 3$ s
- (c) $t = 6$ s



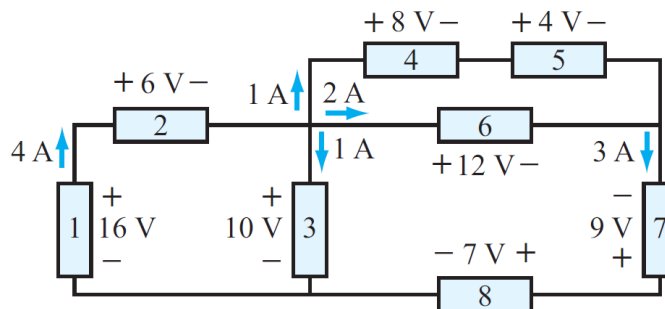
4. For each of the eight devices in the circuit below, determine whether the device is a supplier or a recipient of power and how much power it is supplying or receiving.




Please reproduce and fill in the following table after showing your work:

Device	Supplier or Recipient?	Power [W]
1		
2		
3		
4		
5		
6		
7		
8		

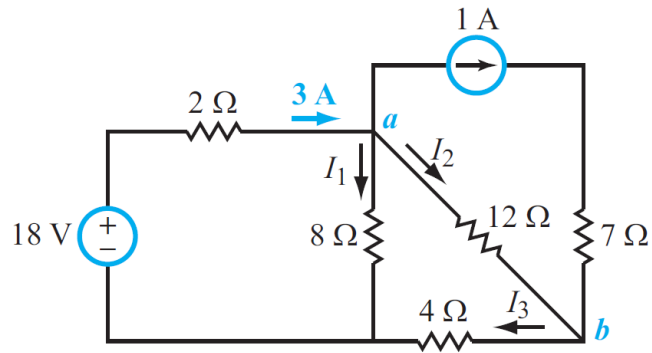5. Determine currents I_1 , I_2 and I_3 in the circuit below.



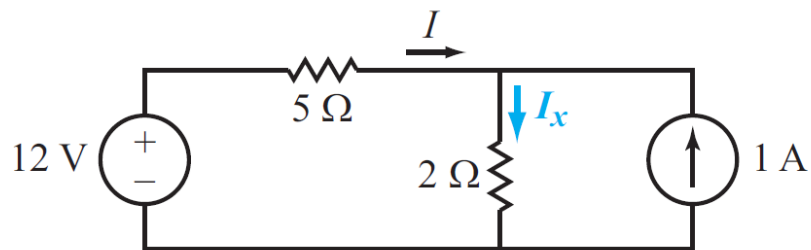6. Determine I_x in the circuit below. Apply KCL once (and provide the equation). Apply KVL once (and provide a second equation). Then provide a solution for I_x .



7. Determine currents I_1 , I_2 , I_3 and I_4 in the circuit below. Again, write KCL and KVL equations, then solve them for the unknown variables.

